

①

AEC

PAGE :

DATE : / /


UNIT-3

Chapter

LARGE SIGNAL AMPLIFIERS.

Classification of Power Amplifiers:

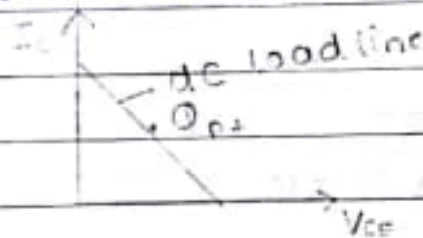- i) Class A amplifier: { Based on the location of Q point on DC load line. }




Q point is located at the centre of dc load line so that it is in the middle of Active region. And collector current I_c due to signal flows for entire cycle of i/p

Hence Conduction 180° ; $\phi_c = 360^\circ$

Conversion efficiency η_c

$$25\% \leq \eta_c \leq 50\%$$

- ii) Class B amplifier:

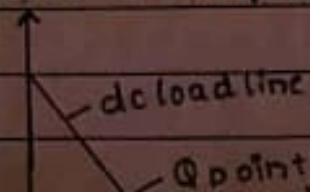

Q-point is located in the cut off region so that the collector current I_c flows for half-cycle of i/p. Hence conduction

REDMI NOTE 5 PRO
MI DUAL CAMERA

Salabhi

(2)

L^e is 180° $\phi_c = 180^\circ$.


$$\eta_c = 78.5\%$$

3 Class AB amplifier.


Q point is located nearer to Cutoff and Collector current flows for more than half cycle of i/p but less than Full cycle of i/p signal.

$$180^\circ < \phi_c < 360^\circ$$

$$50\% < \eta_c < 78.5\%$$

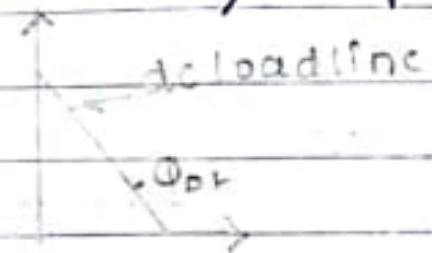

4 Class C amplifier:

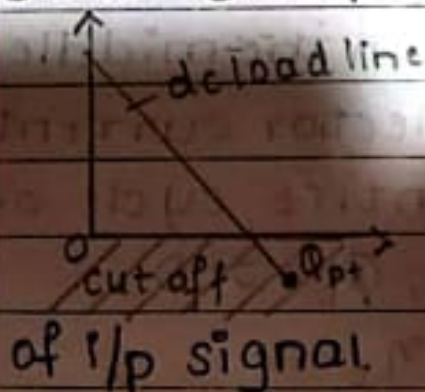

Q point is located deep into cut off region. Hence Collector current flows for less than half cycle

of i/p signal.

$$\phi_c < 180^\circ$$

$$98.5\% > \eta_c > 78.5\%$$

(3)




PAGE :
DATE : / /

Class A Power amplifier:

There are 2 types of class A Power amplifiers.

- Class A amplifier using emitter follower.
- Transformer coupled Power amplifiers.

1 Emitter follower:

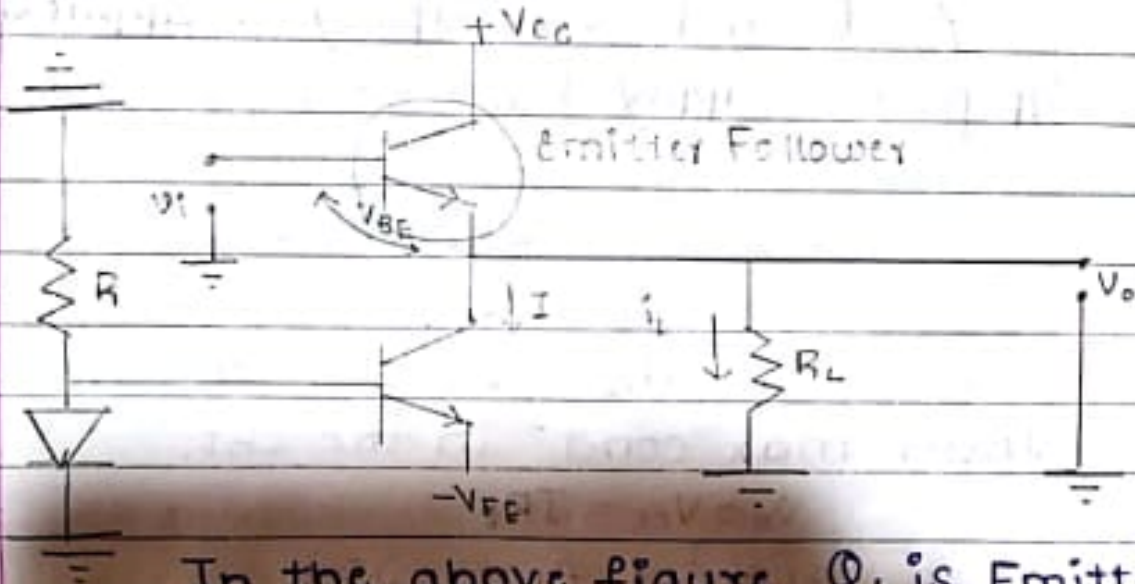

In the above figure Q_1 is Emitter follower and Q_2 is used as Current Mirror in order to get constant current I . It should be noted that whenever i/p voltage changes, Emitter current I_E changes and that change will appear across R_L as o/p voltage.

Let us derive power conversion efficiency for this amplifier.

$$\eta = \frac{P_o}{P_i} \times 100 = \frac{P_{o \text{ acload}}}{P_i} \times 100$$

Solve!

(4)

where P_{oac} across the load is nothing but the voltage v_o has to be taken in terms of rms. Hence

$$V_{o_{acload}} = \left(\frac{v_o}{\sqrt{2}} \right) \frac{1}{R_L}$$

$$= \frac{v_o^2}{2R_L} \quad \text{--- (a)}$$

As Dual Power supply is applied to ckt, i/p power supply $P_{idc} = 2V_{cc} \cdot I$ --- (b)

$$\therefore \eta_c = \frac{v_o^2}{2R_L \times 2V_{cc} I} \times 100$$

$$= \frac{v_o}{R_L} \cdot \frac{v_o}{V_{cc} \cdot I} \times \frac{1}{4} \times 100 \quad \text{--- (c)}$$

Under max condⁿ in the ckt,

$$v_o = V_{cc} = IR_L$$


$$\therefore \eta_c = \frac{1}{4} (100) = 25\%$$

For a class A amplifier (emitter follower Power Amp), $V_{cc} = 10V$, $I = 100mA$, $R_L = 100\Omega$, $v_o = 8V_{peak}$

Find a) Power delivered to Load

b) Average power drawn from supply,

c) Power conversion efficiency.

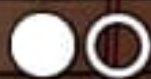

REDMI NOTE 5 PRO
MI DUAL CAMERA


Solⁿ:

$$a \quad P_{oac} = \frac{V_o^2}{2R_L} = \frac{8}{2(100)} = 0.32W.$$

$$b \quad P_{dc} = 2V_{cc} \times I \\ = 2(10)(100 \times 10^{-3}) \\ = 2W.$$

$$c \quad \% \eta_c = \frac{P_{oac}}{P_{dc}} \times 100 \\ = \frac{0.32}{2} \times 100 \\ = 16\%.$$

2 Transformer Coupled Power Amplifier.

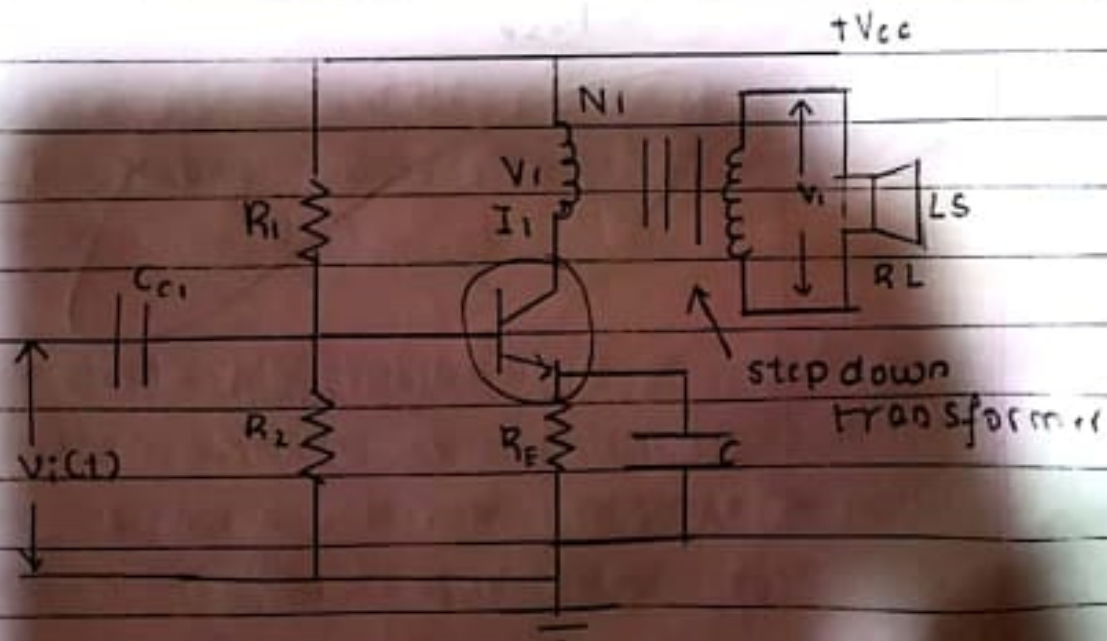

REDMI NOTE 5 PRO
MI DUAL CAMERA

Ckt diagram.

(6)

Analysis.

WKT,

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \text{--- (1)} \quad \& \quad \frac{I_1}{I_2} = \frac{N_2}{N_1} \quad \text{--- (2)}$$

$$\text{(1)} \div \text{(2)},$$

$$\frac{V_1 I_2}{V_2 I_1} = \frac{N_1}{N_2} \times \frac{N_1}{N_2} = \left(\frac{N_1}{N_2} \right)^2 \quad \text{--- (3)}$$

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \left(\frac{N_1}{N_2} \right)^2 \quad \text{--- (4)}$$

where $\frac{V_1}{I_1} \rightarrow$ effective Load Resistance at

collector denoted by R_L'

$$\therefore \text{effective } R_L' = \left(\frac{N_1}{N_2} \right)^2 R_L \quad \text{--- (5)}$$

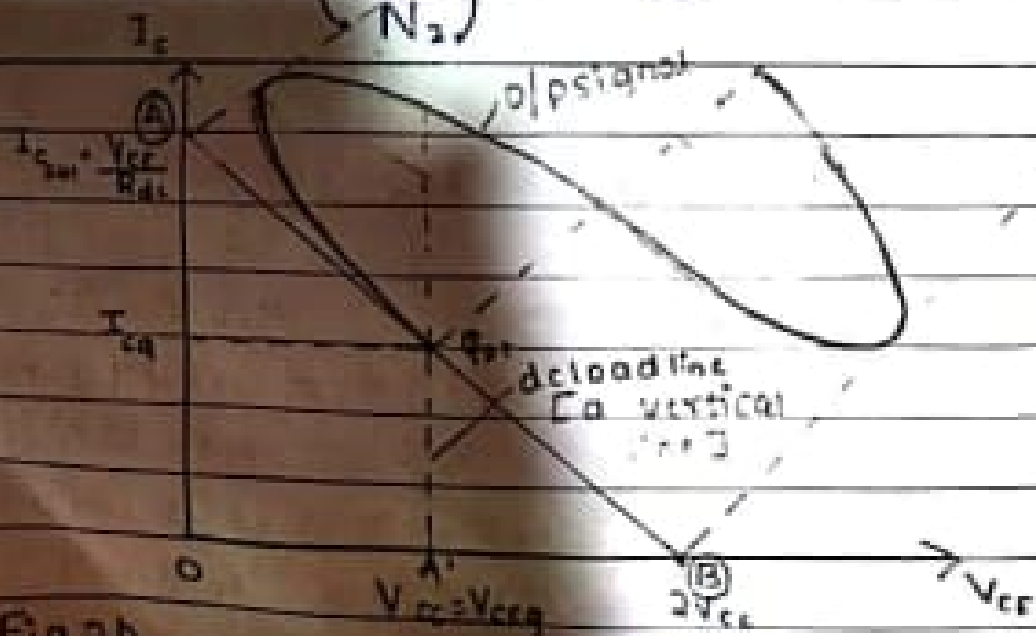


Fig 26

7



PAGE :
DATE : / /

For AC load line, considering the collector part of ckt, along with emitter part with V_{CE} voltage across Collector and Emitter terminals and considering R_{ac} as effective ac resistance of primary winding whose dc resistance is assumed to be 0. As seen from diagram, emitter terminal is directly grounded for AC signal.

Hence we can write the following eq:

$$V_{CC} = I_C R_{ac} + V_{CE} \quad (1)$$

$$V_{CE} = 0$$

$$I_{C_{sat}} = \frac{V_{CC}}{R_{ac}} \quad \text{--- pt A } \left. \vphantom{\frac{V_{CC}}{R_{ac}}} \right\} \text{ac load line}$$

Note: When $I_C = 0$, inductor opposes change.
{ back emf is produced in the dirⁿ opp to cause i.e. V_{CC} }

When $I_C = 0$, because of inductor this current won't become 0. Instead back emf is produced in order to oppose this change by which it has been produced.

$$\therefore \epsilon_b = -V_{CC} = I_C R_{ac}$$

\therefore (1) can be written as, $V_{CC} = -V_{CC} + V_{CE}$

$$V_{CC} = 2V_{CC}$$

ac
load
line

Scale

(8)

As dc resistance of primary winding is assumed to be 0. in eqⁿ ①, $R_{ac}=0$. Hence

$$V_{ce} = V_{cc} - I_c R_{ac} \quad \text{pt (A')}$$

$$\text{where } V_{ce}=0, I_c = \frac{V_{cc}}{R_{ac}} \quad \text{but } R_{ac}=0 \quad \left. \begin{array}{l} \text{dc} \\ \text{load} \\ \text{line} \end{array} \right\}$$

$$\therefore I_c = \infty \quad \text{pt (B')}$$

Hence dc load line is vertical load line $V_{ceQ} = V_{cc}$ as shown in fig ② b.

The intersection of ac & dc load line is operating or Q pt. & o/p signal varies about this Q pt as shown in fig ② b.

Power conversion efficiency.

$$P_{i_{dc}} = V_{cc} I_c \quad \text{--- (a)}$$

$$P_{o_{ac}} = \left(\frac{V_o}{\sqrt{2}} \right)^2 \times \frac{1}{R_L} = \frac{V_o^2}{2R_L} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \\ = \frac{V_m I_m}{2} \quad \text{--- (b)}$$

$$\therefore \eta_c = \frac{P_{o_{ac}}}{P_{i_{dc}}} \times 100 = \frac{V_m I_m}{V_{cc} I_c} \times \frac{1}{2} \times 100 \quad \text{--- (c)}$$

for max η_c , $V_m = V_{cc}$ & $I_m = I_c$.

$$\therefore \eta_{c_{max}} = 50\%$$

(9)



PAGE:

DATE: / /

1. A transformer coupled class A ^{power} amplifier has a current of 200mA from a collector supply of 10V when no signal is applied to it. Determine max i/p power, max collector efficiency if load connected across transformer secondary is 2Ω & turns ratio is 5:1.

Solⁿ: $I_{dc} = 200\text{mA}$.

$$R_L = 2\Omega.$$

$$V_{dc} = V_{cc} = 10\text{V}.$$

$$P_{dc} = I_{dc} \times V_{dc} = 200 \times 10^{-3} \times 10 \\ = 2\text{W}.$$

$$P_{ac} = \left(\frac{I_m}{\sqrt{2}} \right)^2 R_L' \quad (I_m = I_c = 200\text{mA})$$

$$R_L' = \left(\frac{N_1}{N_2} \right)^2 R_L$$

$$= 5^2 (2) = 50\Omega.$$

$$P_{ac} = \left(\frac{200 \times 10^{-3}}{\sqrt{2}} \right)^2 50 = 1\text{W}.$$

$$\therefore \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{1}{2} (100)$$

$$= 50\%.$$

(10)

Class B transformer coupled amplifier or Push-pull transformer.

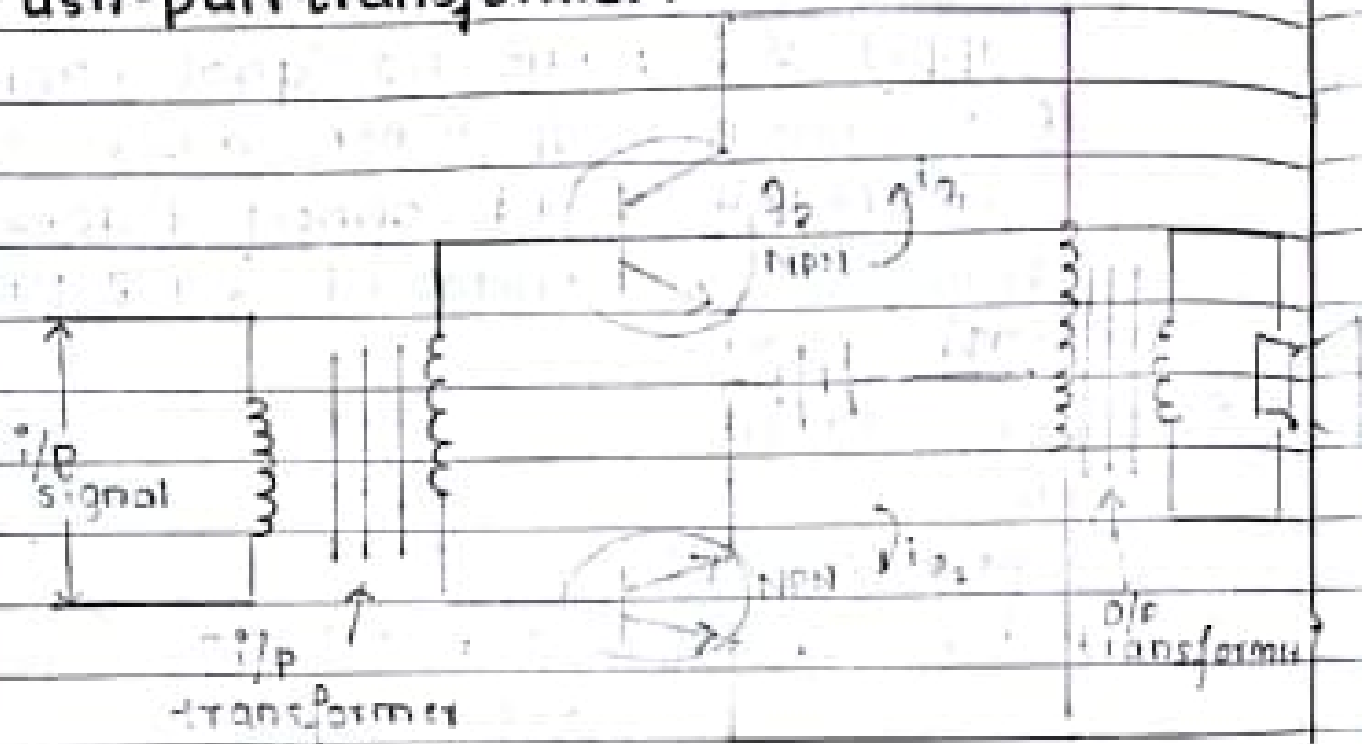


Fig 2a



(11)



PAGE:

DATE: / /

o/p DC Power denoted as $P_{oac} = V_{rms} \cdot I_{rms}$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$= \frac{V_m I_m}{2} \quad \text{--- (1)}$$

i/p DC power supplied

$$P_{iac} = I_{ac} \cdot V_{dc}$$

But as o/p current is like full wave rectified o/p, avg current I_{ac} is given by $\frac{2I_m}{\pi}$

Hence, $P_{iac} = \frac{2I_m}{\pi} \cdot V_{dc}$

$$\therefore \eta_c = \frac{P_{oac}}{P_{iac}} \times 100$$

$$= \frac{1}{2}$$

$$\frac{I_m V_m}{2} \times \frac{\pi}{2 I_m V_o}$$

$$= \frac{\pi}{4} \times \frac{V_m}{V_{cc}} \times 100$$

To get max conversion efficiency $V_m = V_{cc}$.

$$\therefore \eta_{max} = \frac{\pi}{4} (100)$$

$$= 78.5\%$$

(12)


1. In class B power amplifier, $V_{cc} = 50V$ & o/p voltage = $45V_{peak}$. Determine Conversion efficiency of this amplifier.

Solⁿ: $\% \eta_c = \frac{\pi}{4} \times \frac{V_m}{V_{cc}} \times 100.$


$$= \frac{\pi}{4} \times \frac{45}{50} \times 100.$$

$$= 70.68\%.$$

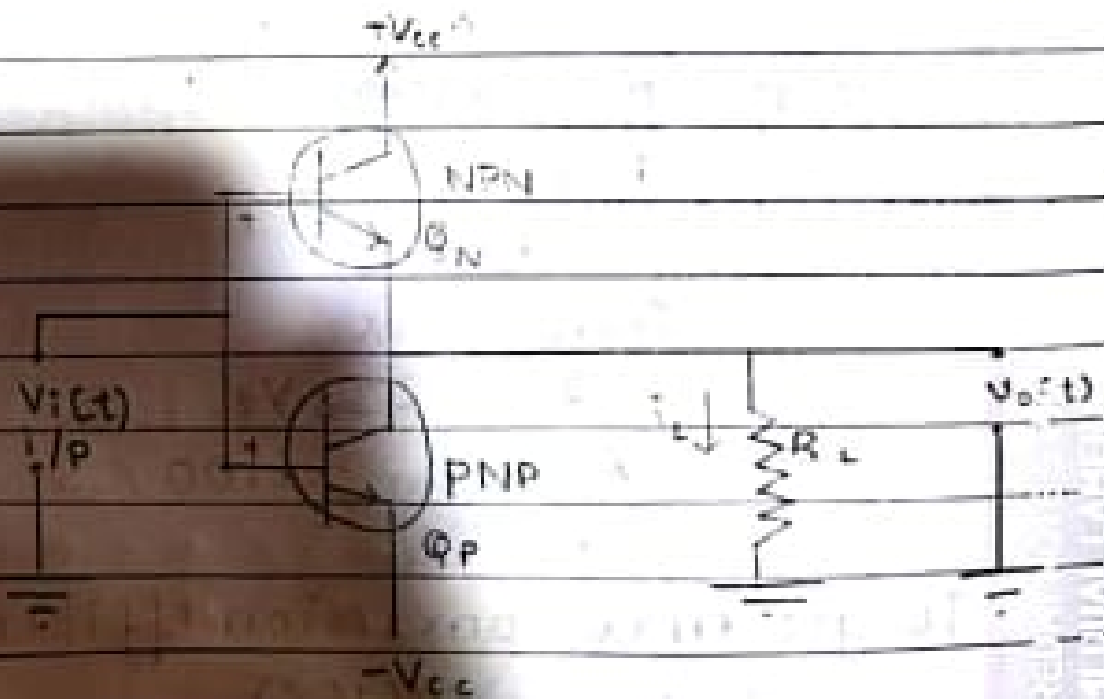Transformless Class B Power Amplifier.
[Complementary Amplifier].



Dual Power Supply

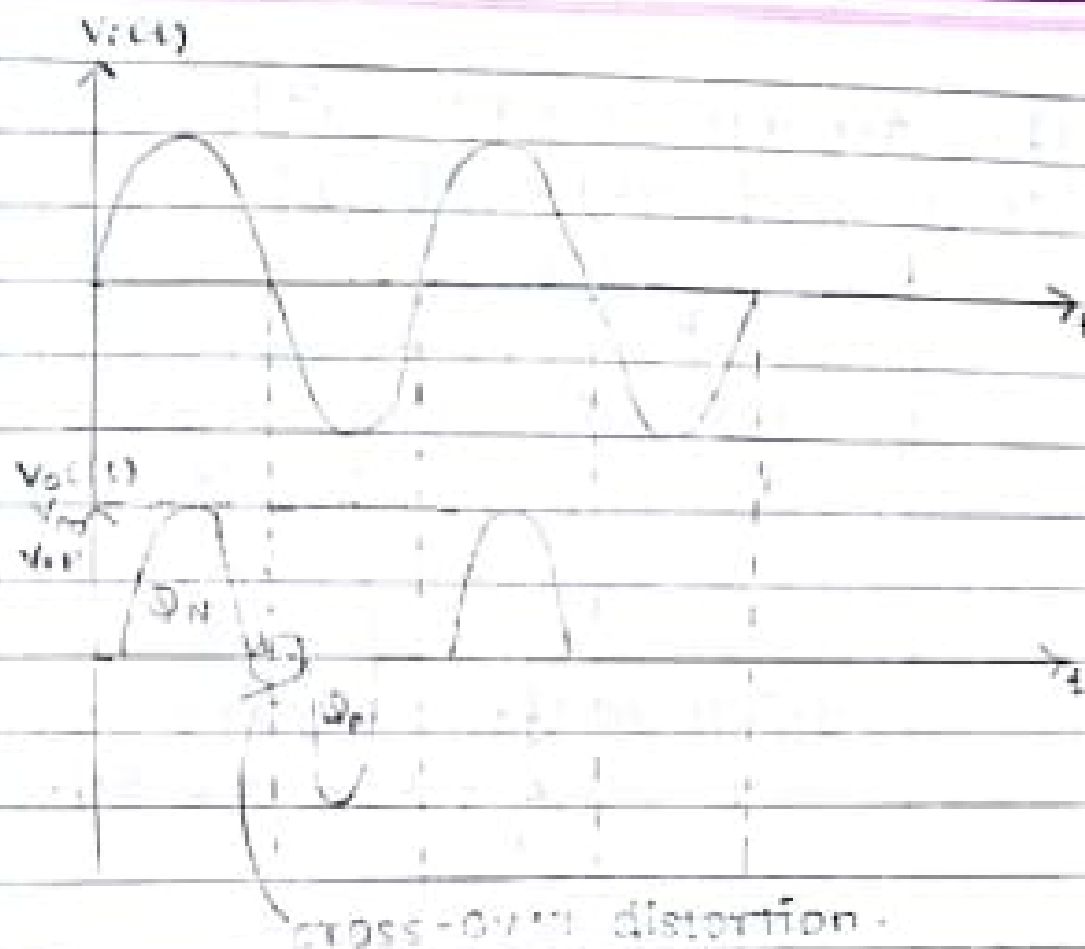

Power conversion efficiency:

Let V_m be the peak value of o/p signal
 then $P_{oac} = \left(\frac{V_m}{\sqrt{2}} \right)^2 \times \frac{1}{R_L}$
 $= \frac{V_m^2}{2R_L} \quad \text{--- (1)}$

As there is a Dual Power Supply, P_{dc} will be equal to $2(I_{dc} \times V_{cc})$.

$$P_{dc} = 2V_{cc} \cdot I_{dc}$$

$$= 2I_{dc} V_{cc} \quad \text{--- (2)}$$

(14)

I_{dc} - Average current written as $V_m/\pi R_L$ as the avg of only half-cycle is taken.

$$\therefore P_{dc} = \frac{2V_m}{\pi R_L} \times V_{cc} \quad (3)$$

$$\begin{aligned} \therefore \% \eta_c &= \frac{P_{dc}}{P_{ac}} \times 100 = \frac{V_m R_L}{2 R_L} \times \frac{\pi R_L}{2 V_m \times V_{cc}} \\ &= \frac{\pi}{4} \frac{V_m}{V_{cc}} \times 100 \quad (4) \end{aligned}$$

To get max efficiency $V_m = V_{cc}$.

$$\therefore \% \eta_{max} = \frac{\pi}{4} (100) = 78.5\%$$

Determine dc power supplied to the ckt of transformer less class B power amplifier. Output power delivered to the load & power conversion efficiency when o/p peak voltage is 2.6V & $V_{cc} = 3V$, $R_L = 1K\Omega$.

$$\% \eta_c = \frac{\pi}{4} \times \frac{2.6}{3} \times 100 = \frac{P_{dc}}{P_{ac}}$$



$$P_{dc} = \frac{2V_m}{\pi R_L} \times V_{cc} = 4.96 \text{ mW}$$



$$P_{oac} = \frac{V_m}{2R_L} = 3.38 \text{ mW}$$



$$\therefore \eta_c = 68\%$$

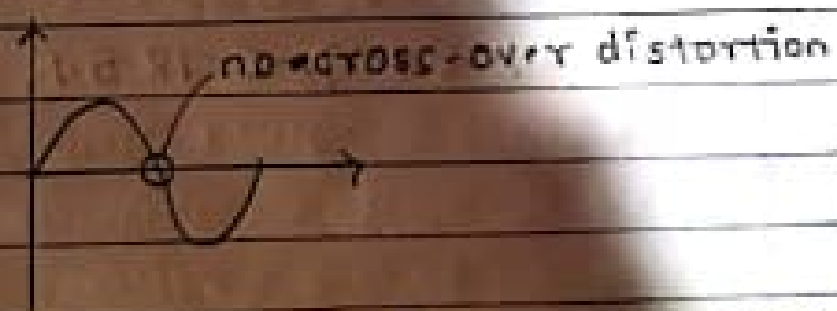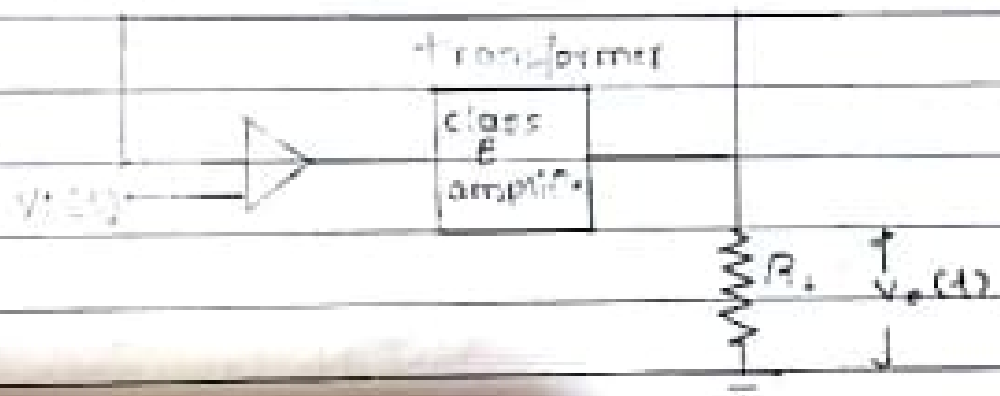To eliminate cross over distortion using opamp as an amplifier as shown in the below figure, then o/p across R_L will be without any cross over distortion.



Other way of reducing cross-over distortion is by applying biasing for both transistors as shown below. But this circuit is no longer a class B power amplifier; it is class AB amplifier.



(16)

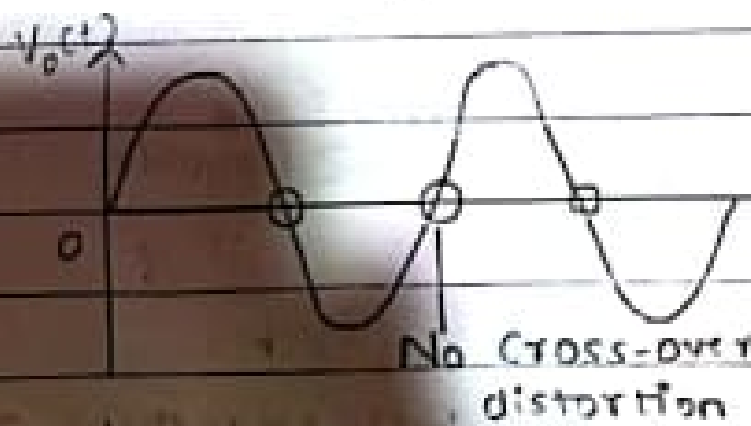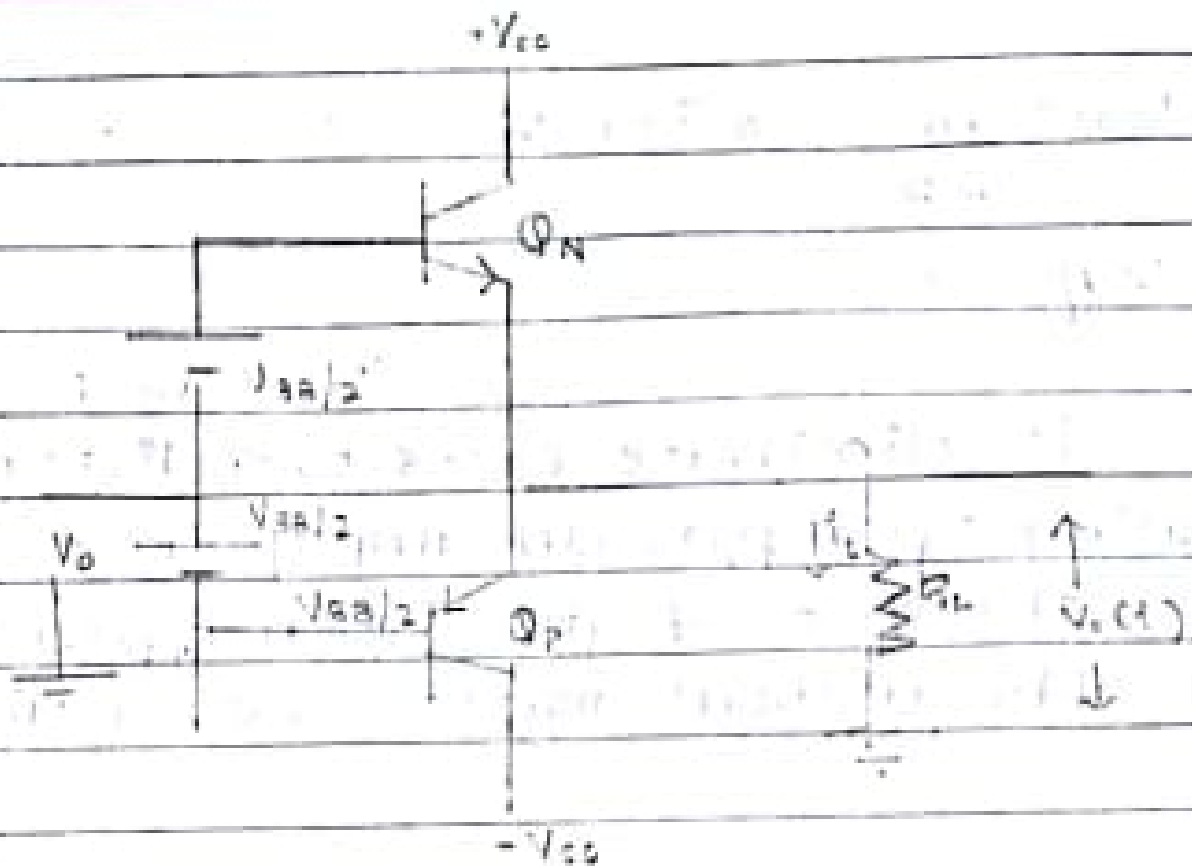

$$50.1\% < \eta_c < 78.5\%$$



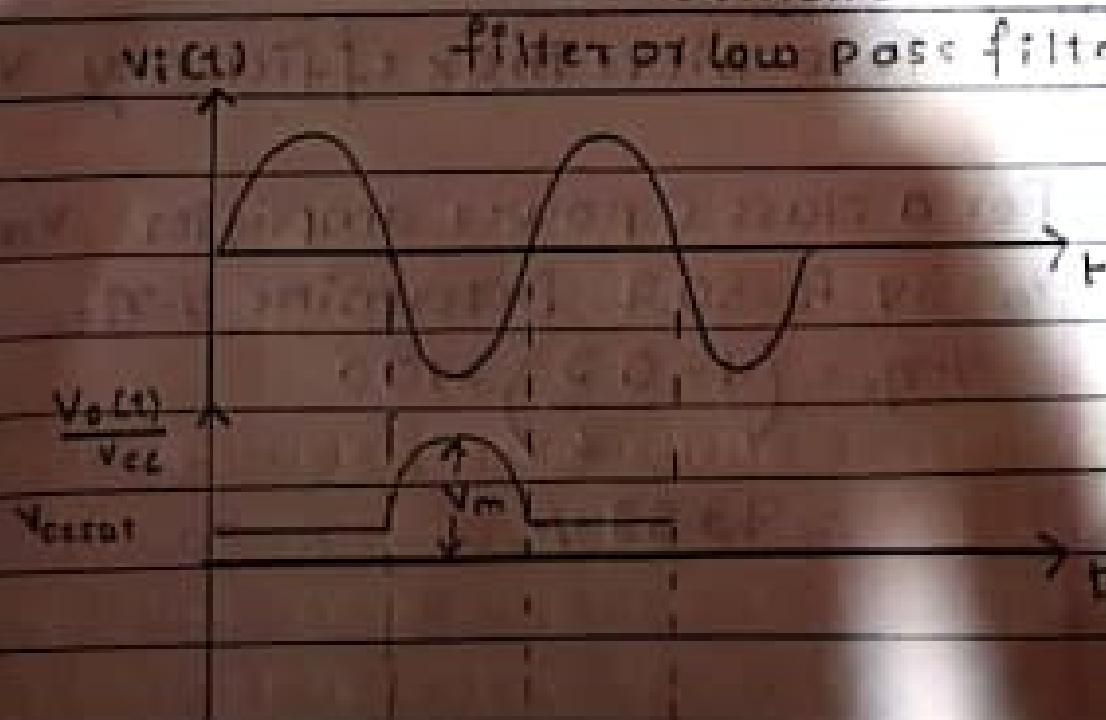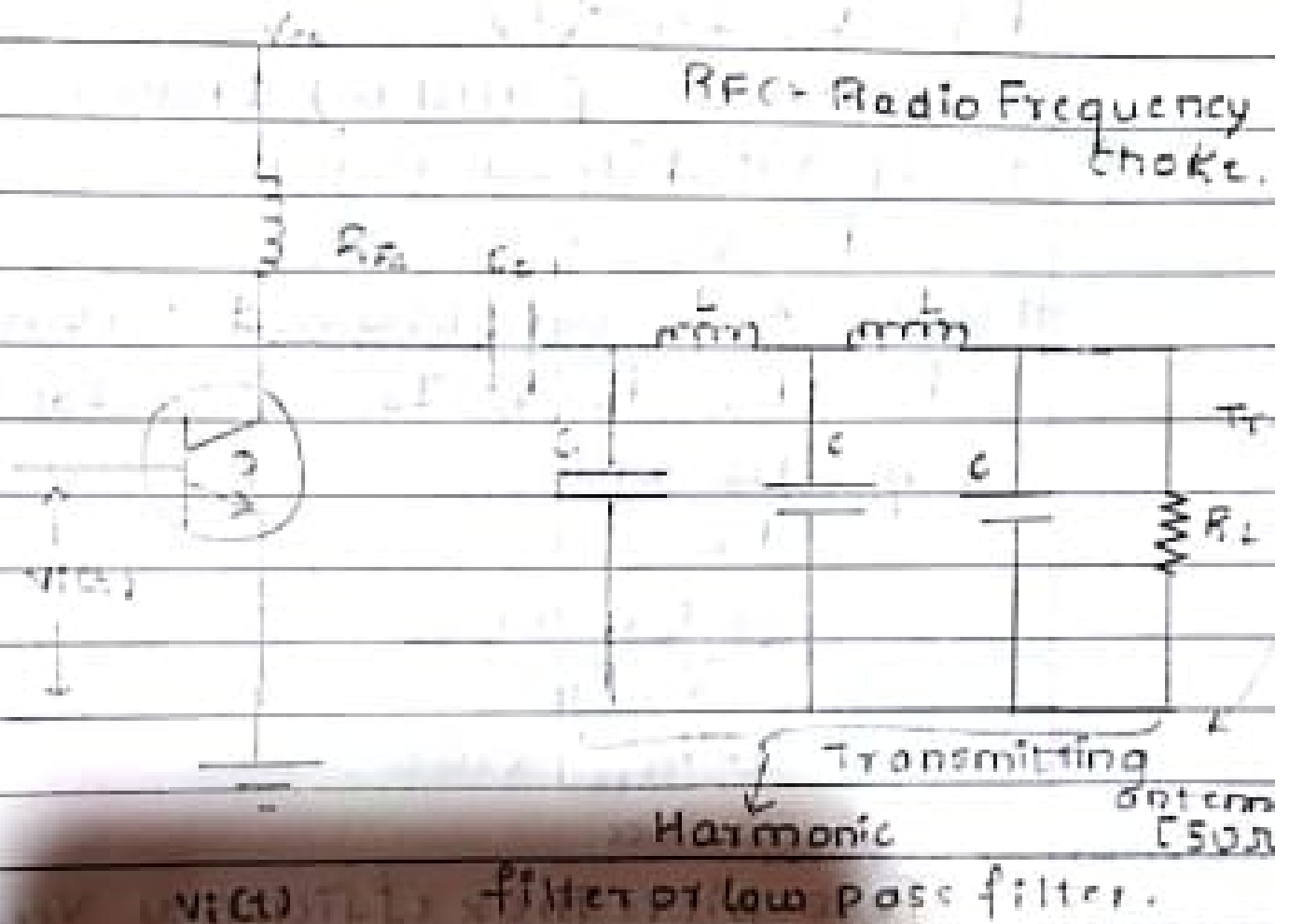Class C Power amplifier [Class C o/p stage].



Power conversion efficiency.

Input dc power supplied to ckt

$$P_{idc} = V_{cc} I_{dc} \quad (1)$$

Power dissipated by transistor, when it is operated in sat region.

$$P_T = V_{CEsat} \times I_{dc} \quad (2)$$

then o/p AC power obtained across the load

$$P_{oac} = P_{idc} - P_T = V_{cc} I_{dc} - V_{CEsat} I_{dc} \quad (3)$$

$$\therefore \eta_c = \frac{P_{oac}}{P_{idc}} \times 100$$

$$= \frac{I_{dc} (V_{cc} - V_{CEsat})}{V_{cc} I_{dc}}$$

$$= 1 - \frac{V_{CEsat}}{V_{cc}} \times 100$$

To achieve max efficiency $V_{CEsat} \ll V_{cc}$

For a class C power amplifier, $V_{CEsat} = 0.2V$,
 $V_{cc} = 3V$, $R_L = 50\Omega$. Determine $\therefore \eta_c$.

$$\begin{aligned} \text{Sol}^n: \quad \therefore \eta_c &= \left(1 - \frac{0.2}{3} \right) \times 100 \\ &= 93.33\% \end{aligned}$$