

Network Theorems

Applicable to linear systems: obeys


① principle of homogeneity (scaling)

② principle of Superposition.

$$\text{If } kx(t) \Rightarrow ky(t)$$



$x(t)$

excitation

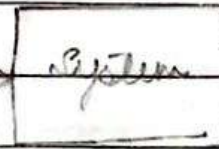

$y(t)$
response
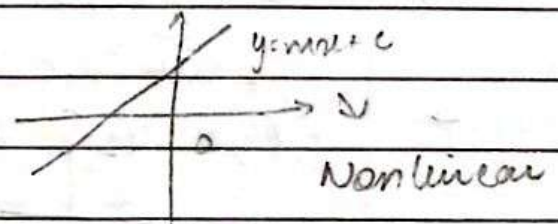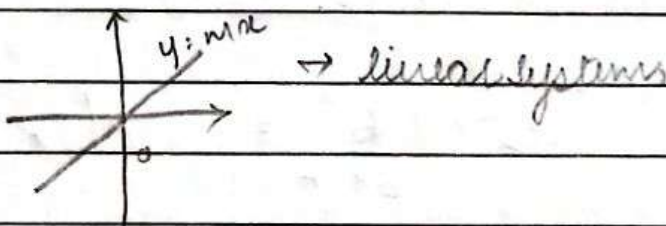
$$\alpha x_1(t) + \beta x_2(t) \Rightarrow \alpha y_1(t) + \beta y_2(t)$$




Network Theorem:

- 1) Law of Superposition
- 2) Thevenin's Theorem
- 3) Norton's Theorem
- 4) Maximum power transfer Theorem
- 5) Reciprocity Theorem


① \downarrow Superposition Theorem

Deactivate independent voltage source \rightarrow S/C

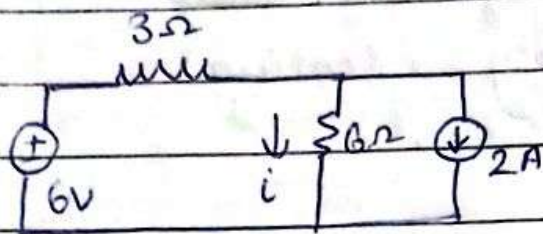- Determine the current in 6Ω resistor in the network using the principle of superposition.




① Deactivating 6V source. (5/c)

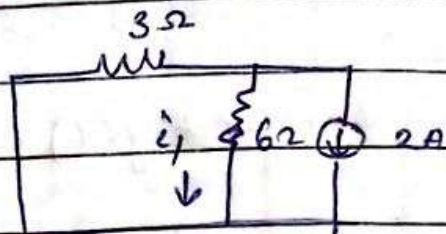

$$i_1 = \frac{2 \times 3}{6+3} = \frac{6}{9} = \frac{2}{3} A$$


② Deactivating 2A current source. (0/c)

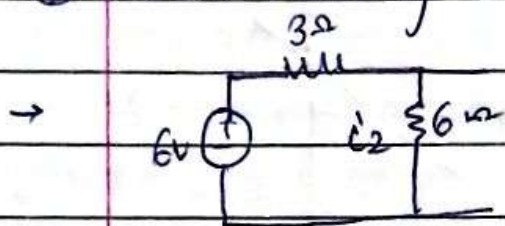

$$i_2 = \frac{6}{3+6} = \frac{2}{3} A$$

$$i = i_1 + i_2 = \frac{2}{3} + \frac{2}{3} = \frac{4}{3} A$$

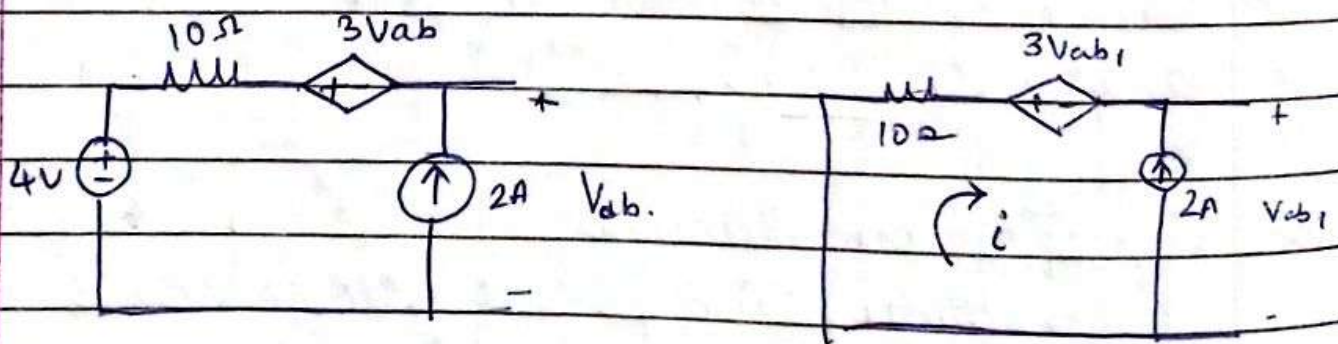
- Use superposition principle to find terminal voltage V_B in the following circuit.



$$-i \times 10 - 3V_{ab1} - V_{ab1} = 0$$

$$-i \times 10 - 4V_{ab1} = 0 \Rightarrow -(2) \times 10 - 4V_{ab1} = 0$$

$$V_{ab1} = -5V$$

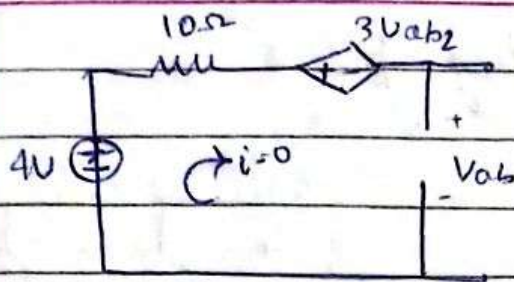


$$4 - i \times 10 - 3V_{ab2} - V_{ab2} = 0$$

$$4 - 4V_{ab2} = 0$$

$$V_{ab2} = 1V$$



$$V_{ab} = V_{ab1} + V_{ab2} = 5 + 1 = 6V$$

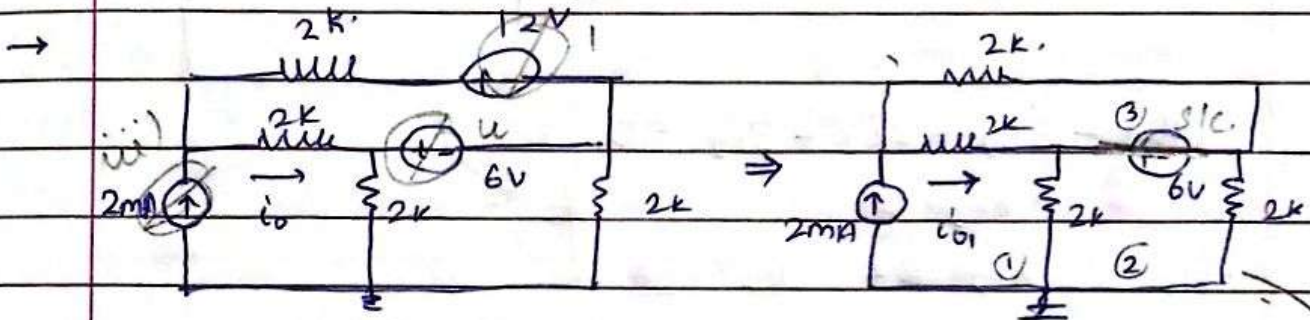- Use superposition principle to find the current i_o in the following circuit.



In loop 1, $i_{o1} = 2mA$

$$i_{o1}' = \frac{12}{4} = 3mA$$

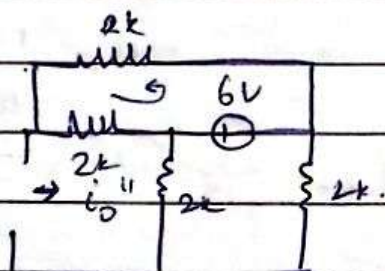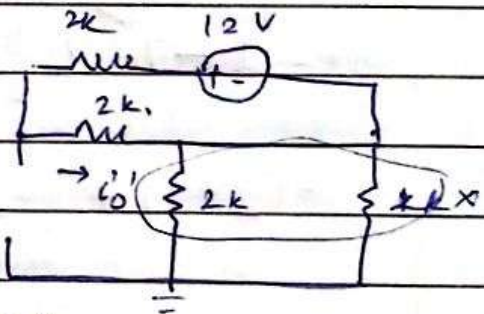


$$i_{o1}'' = \frac{6}{4} = 1.5mA$$



$$i_{o1}''' = 2mA$$


$$i_{o1}''' = 1mA \text{ at } 2k \text{ resistor}$$

$$= \frac{2 \times 2}{2+2} = 1mA$$

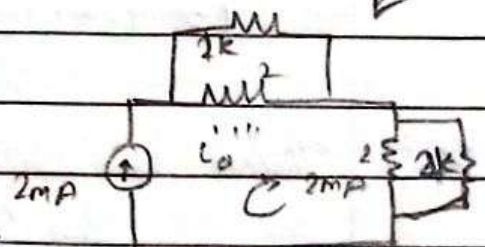


$$i_o = \frac{+3 + 3}{2} + 1 = 2.5mA$$

• Determine current i using p.s

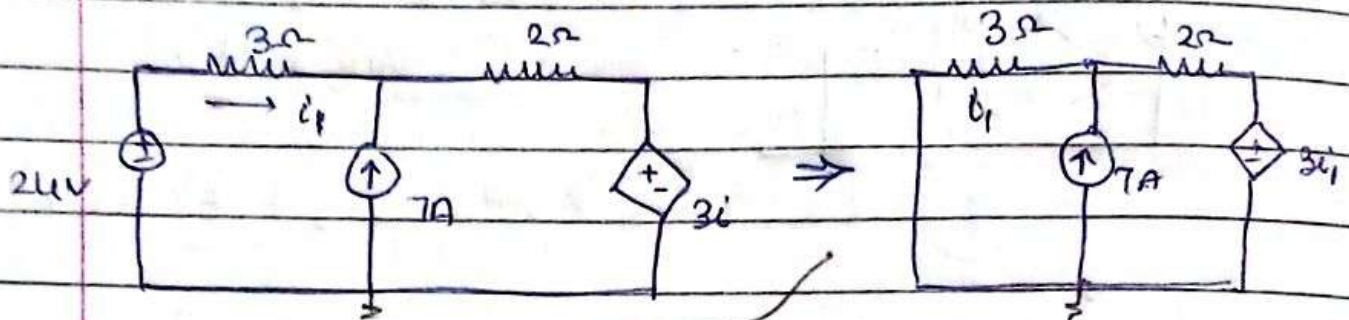
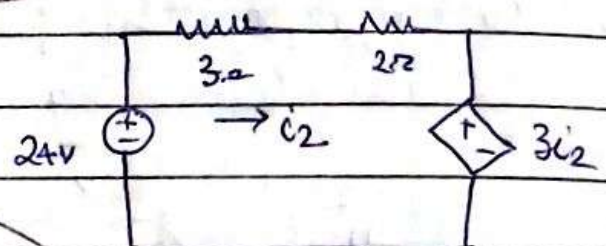
$$i_1 = \frac{2 \times 7}{3+2} = -\frac{14}{5} \text{ A}$$



$$24 - 3i_2 - 2i_2 - 3i_2 = 0$$

$$24 - 8i_2 = 0$$

$$8i_2 = 24 \quad i_2 = 3 \text{ A}$$

$$V = -3i_2$$

$$-i_2 - 7 + \frac{V - 3i_2}{2} = 0$$


$$-i_2 - 7 + \frac{-3i_2 - 3i_2}{2} = 0 \Rightarrow -4i_2 - 7 = 0$$

$$-4i_2 = 7$$

$$i_2 = -\frac{7}{4} \text{ A}$$

$$i = i_1 + i_2 = -\frac{14}{5} - \frac{7}{4} = -\frac{59}{20} \text{ A}$$


✓ 2) Thevenin's Theorem.

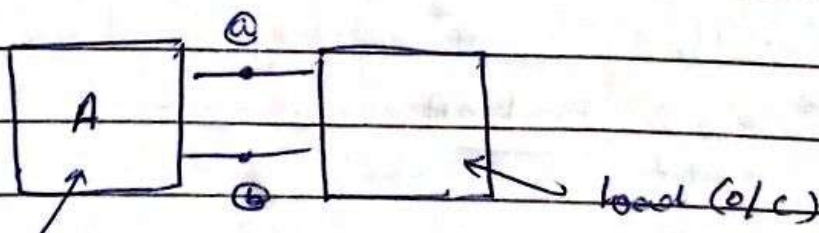

Thevenin's Eq like.

V_{th} & R_{th}

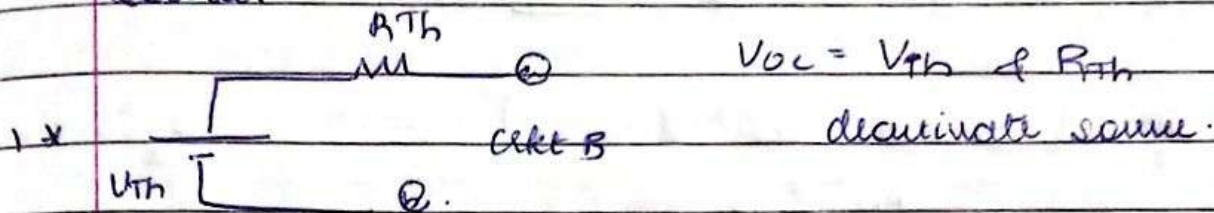
- 1) when circuit has only resistors & independent sources.
- 2) when circuit has only resistors, dependent & independent.
- 3) when circuit has only resistors & only dependent sources.



2x $V_{Th} = V_{oc}$; $I_{sc} = i_{sc}$; $R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{Th}}{I_{sc}}$

3x $R_{Th} = \frac{V_{test}}{1A}$

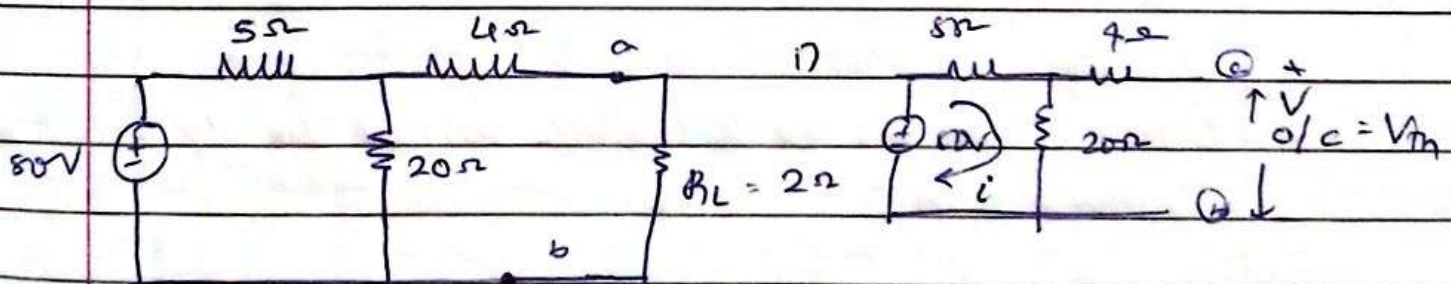
➤ Using Thevenin's Theorem, determine current i flowing through $R_L = 2\Omega$ in foll ckt




$I = \frac{50}{20+5} = 2A$; $V_{oc} = V_{20\Omega} = I \times 20 = 2 \times 20 = 40V$

⑦ Deactivating the 50V source

$R_{Th} = 20 \parallel 5 + 4 = 8\Omega$

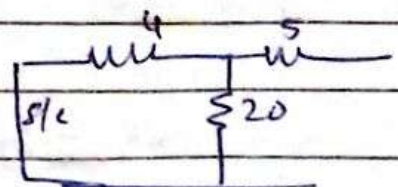


Use the Thevenin's eq.ckt is,

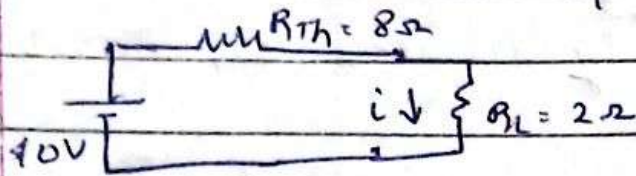

$$i = \frac{V_{Th}}{R_{Th} + R_L} = \frac{40}{8+2} = 4A$$

$$P_{R_L} = i^2 R_L = 16 \times 2 = \underline{32W}$$

(If it is dependent source)

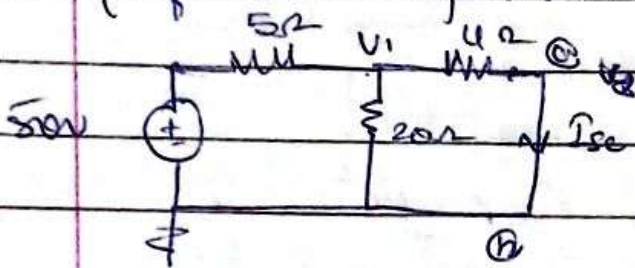

$$\frac{V_1 - 50}{5} + \frac{V_1}{20} + \frac{V_1}{4} = 0$$


$$\frac{V_1}{2} = 10$$

$$V_1 = 20V$$

$$I_{sc} = \frac{V_1}{4} = \frac{20}{4} = 5A$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{40}{5} = 8\Omega$$

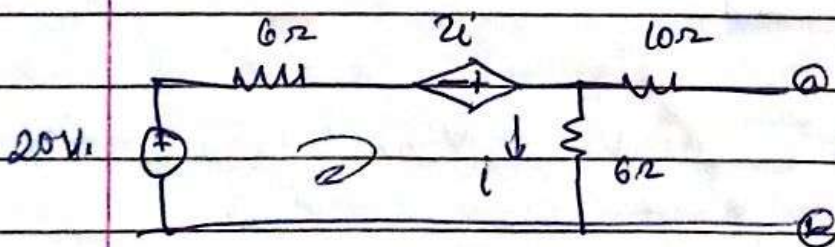2) Draw Thevenin's eq.ckt with respect to o/p circuit terminals a & b



$$20 - 6i + 2i - 6i = 0$$

$$20 - 10i = 0 \Rightarrow i = 2A$$

$$V_{oc} = 2 \times 6 = 12V = V_{th}$$

KCL at node K

$$-I_1 + i + I_2 = 0$$

$$I_2 = I_{sc}$$

$$-I_1 + i + I_2 = 0$$

$$i = I_1 - I_2 \quad (1)$$

loop 1

$$20 - 12I_1 - 12I_2 + 2i + 6I_2 = 0$$

$$20 - 6I_1 - 6(I_1 - I_2) + 2i = 0$$

$$20 - 10I_1 + 4I_2 = 0$$

loop 2

$$-6(I_2 - I_1) - 10I_2 = 0$$

$$6I_1 - 16I_2 = 0$$

$$I_1 = \frac{40}{17} = 2.35A$$

$$I_2 = I_{sc} = 0.8823A$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{12}{0.88} = 13.63\Omega$$

Thevenin's eq ckt is,



Verification

Using Nodal

$$\frac{V_1}{6} + \frac{V_1}{10} + \frac{V_1 - 20}{6} = 0 \quad V_1 = i$$


$$V_1 \left(\frac{1}{6} + \frac{1}{10} + \frac{1}{6} - \frac{20}{36} \right) = \frac{20}{6} \Rightarrow V_1 = \frac{200}{8}$$

$$V_1 = 8.82V$$

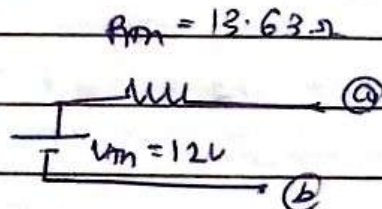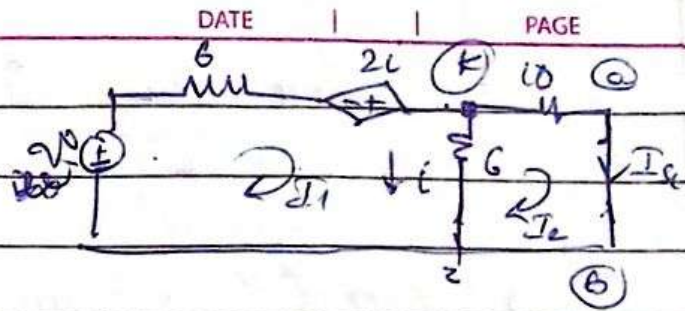

$$I_{sc} = \frac{V_1}{10} = \frac{8.895}{10} = \underline{\underline{0.88}}$$

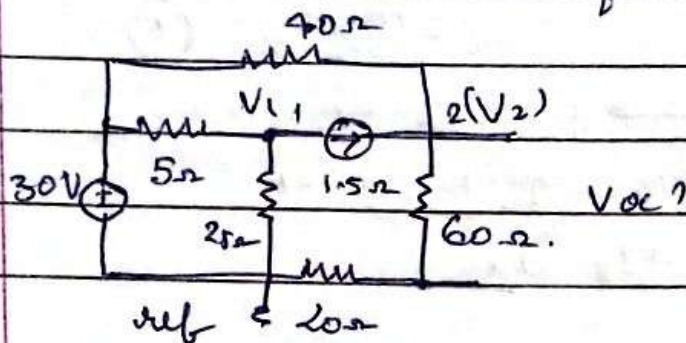- 3) Determine Thevenin & Norton across of a circuit terminals a & b in full ckt




At node 1;

$$\frac{V_1 - 30}{5} + \frac{V_1}{25} + 1.5 = 0 \Rightarrow V_1 = 18.75$$


At node 2;

$$\frac{V_2}{60} + \frac{V_2 - 30}{40} - 1.5 = 0$$

$$V_2 = \underline{60V}$$

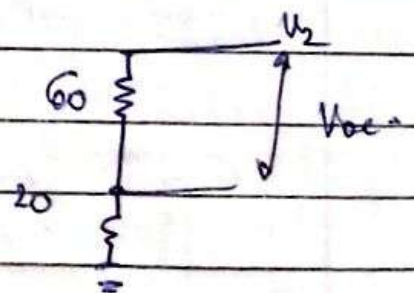

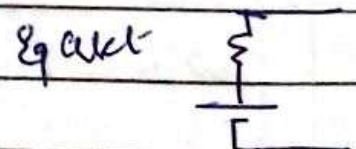
$$i = \frac{V_2}{80} = \frac{60}{80} = 0.75$$




$$V_{oc} = i \times 60 = 45V = V_{Th}$$

verify
by dc

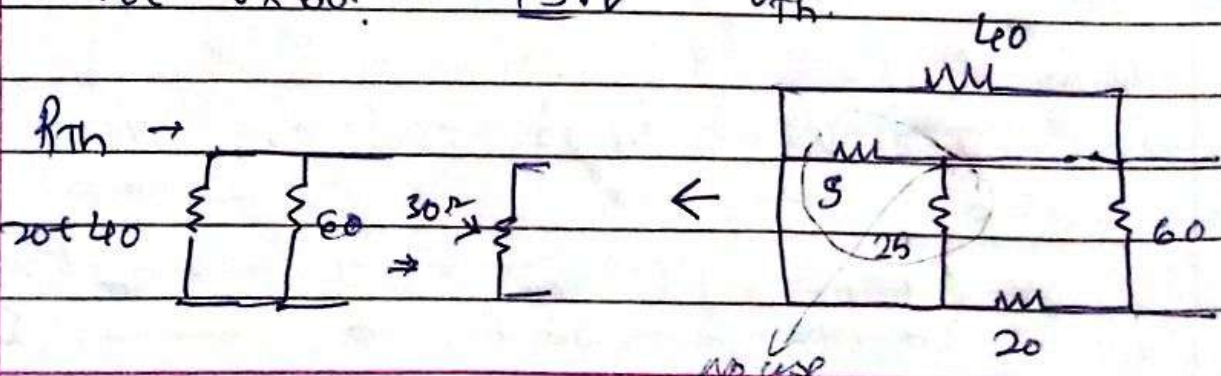

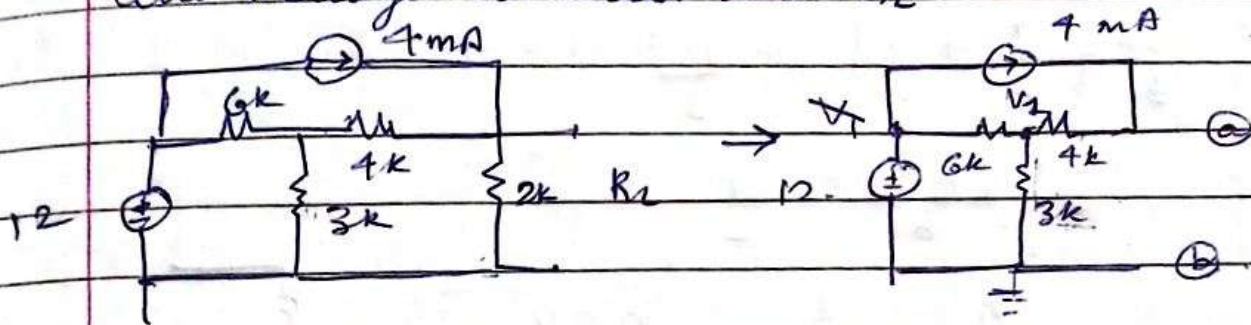Use T.T to determine T.E.C parameters for the following ckt with R_L of $2k\Omega$, also determine the voltage V_o across this $R_L = 2k\Omega$




$$\frac{V_1}{3} + \frac{V_1 - 12}{6} + V_1 = 4$$

$$= V_1 \left(\frac{1}{3} + \frac{1}{6} \right) = 4$$


$$V_1 = 12V, \quad i_1 = \frac{12}{3} = 4mA$$
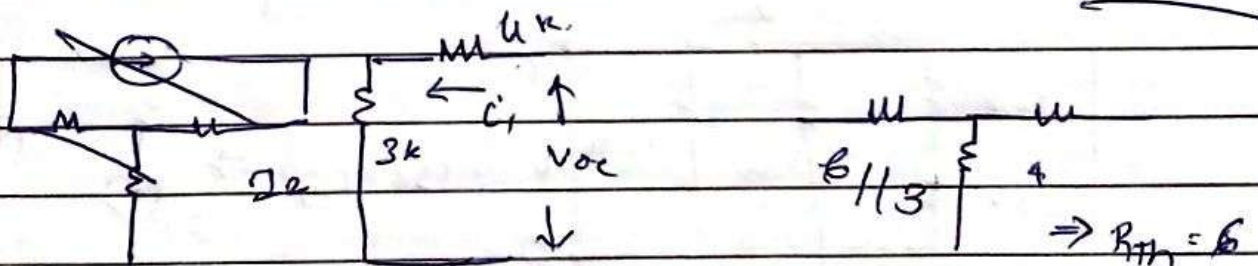
$$V_{oc} = i \times 3 + i \times 4 = 4 \times 3 + 4 \times 4 = 12 + 16 = 28V$$



$$V_o = \frac{V_{Th}}{R_{Th} + R_L} \quad R_L = 2k\Omega$$

⑤ Find T.E.C for the ckt.

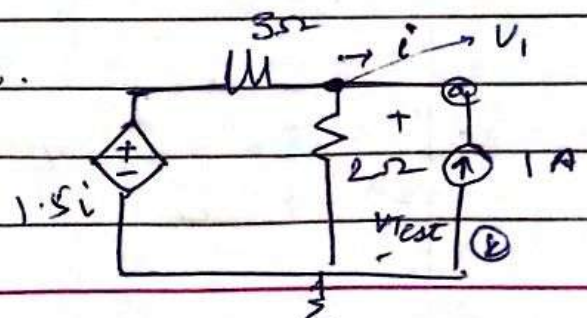


$$\frac{V_1}{2} + \frac{V_1 - 1.5}{3} - 1 = 0$$

$$\frac{V_1}{2} \left(\frac{1}{2} + \frac{1}{3} \right) + \frac{1.5}{3} - 1 = 0$$

$$\frac{V_1 \times 5}{6} = \frac{1}{2}$$


$$V_1 = \frac{6}{10} = 0.6V$$
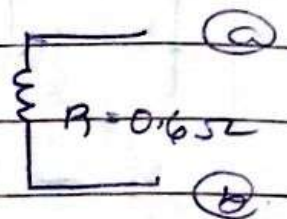
$$R_{th} = \frac{V_{test}}{I_A} = \frac{0.6V}{1A} = 0.6\Omega$$





Norton's Theorem.


Draw Norton eq.ckt for the foll. ckt.

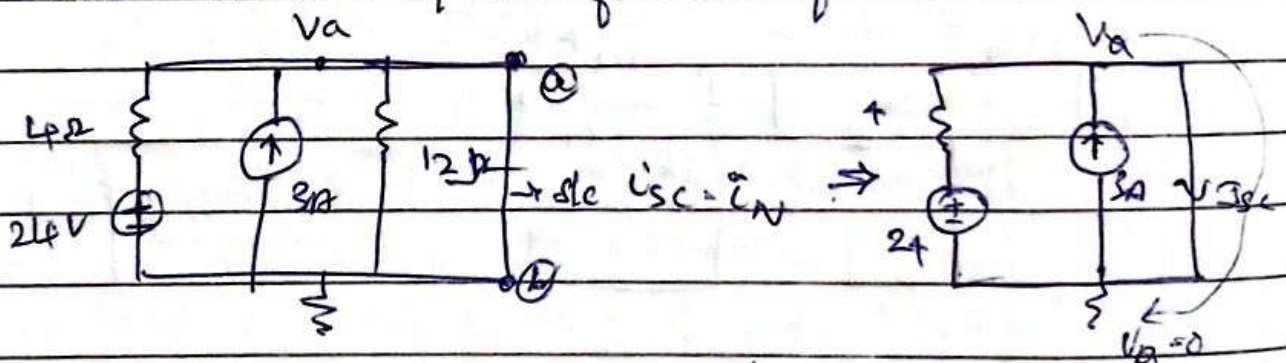

$$\frac{V_a - 24}{4} + 3 - \frac{V_a}{12} = 0$$

$$V_a = 0 \Rightarrow I_{sc} = +9A$$

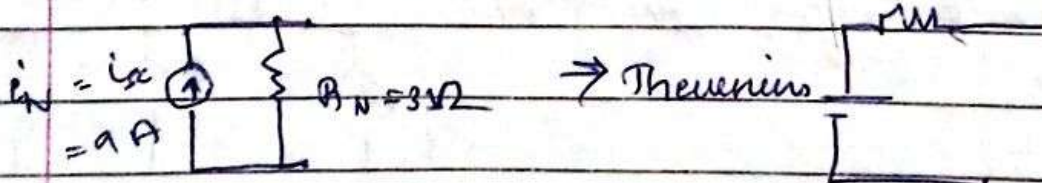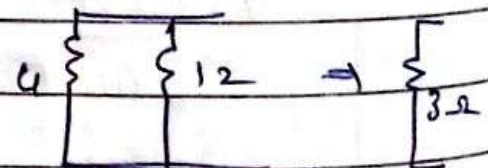

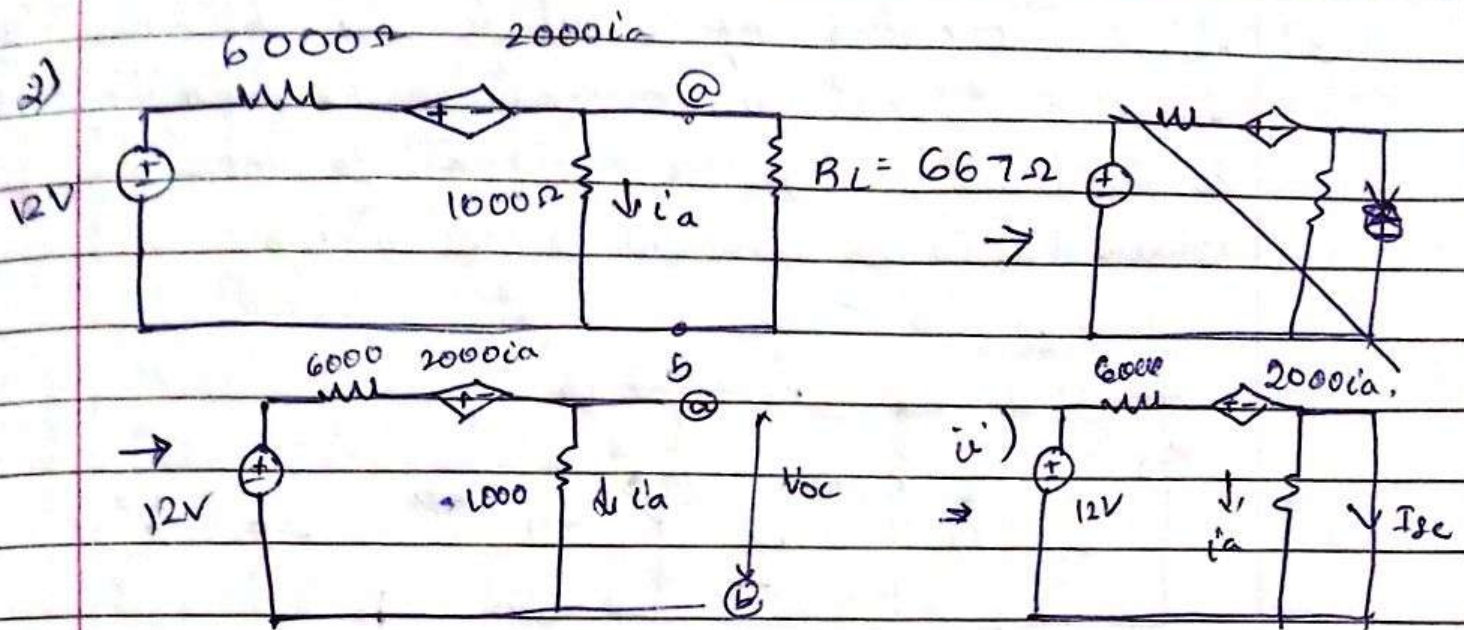


$$12 - i_a(6000 + 1000) - 2000i_a = 0$$

$$12 - 9000i_a = 0$$


$$12 = 9000i_a$$

$$i_a = 1.33 \text{ mA}$$

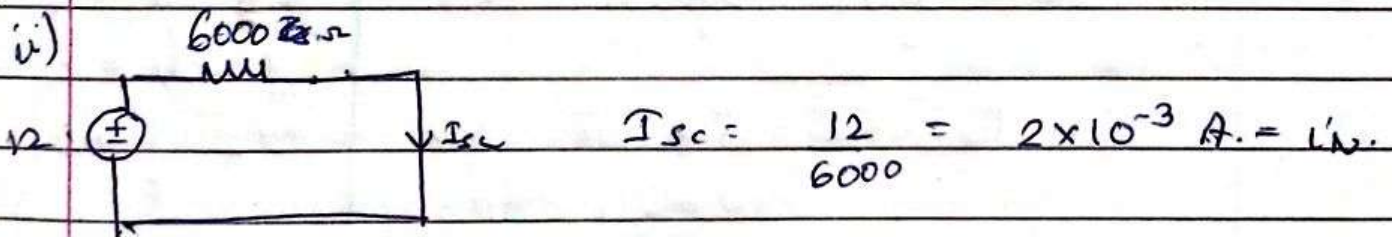
$$V_{oc} = V_{ab} = i_a \times 1000 = 1.33 \text{ V}$$


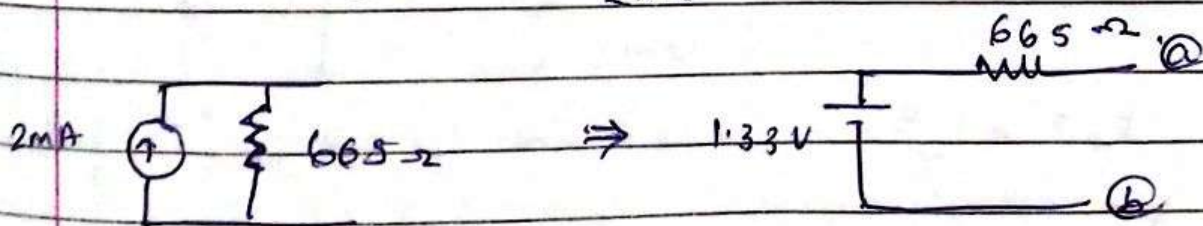
$$R_N = R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{1.33}{2 \times 10^{-3}} = 665 \Omega = R_{Th}$$



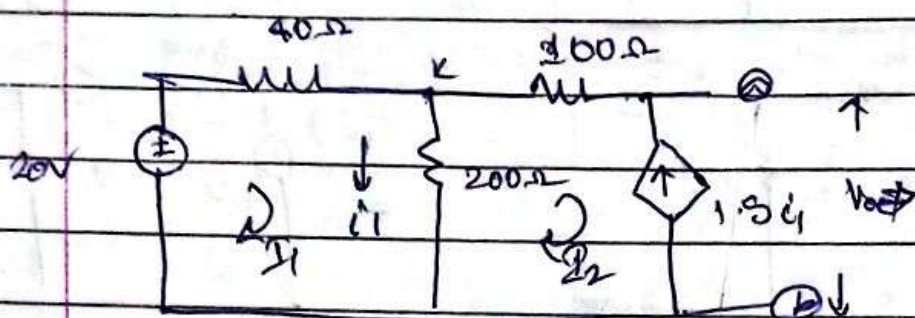- 3) Find Thevenin's eq circuit for the following ckt diagram also draw corresponding Norton's eq ckt & determine the power delivered to 100Ω load resistor which has to be connected across a & b



$$I_b = -1.5 i_1$$

Applying KVL

$$20 - 40I_1 - 200I_1 + 200I_2 = 0$$

$$200I_2 - 240I_1 = -20$$

$$-200I_2 + 200I_1 - 100I_2 = 0$$

$$I_2 = \frac{200I_1}{300} = \frac{2I_1}{3}$$

$$200 \cdot \frac{2I_1}{3} - 240I_1 = -20$$

$$133.33I_1 - 240I_1 = -20$$

$$-106.67I_1 = -20$$

$$I_1 = 0.187$$

$$I_2 = \frac{2}{3} \times 0.187$$

$$= 0.1246$$

$$I_2 = -1.5 i_1$$

KU at k

$$-I_1 + i_1 + I_2 = 0$$

$$i_1 = I_1 - I_2$$

loop 2

$$I_2 = -1.5 i_1$$

$$-0.5 I_2 = -1.5 I_1$$


$$I_2 = \frac{1.5}{0.5} I_1 = 3I_1$$

$$I_1 = -\frac{0.5}{9}$$

$$I_2 = 3I_1$$

$$I_2 = -\frac{1.5}{9}$$

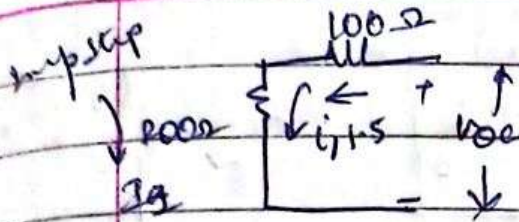
$$\Rightarrow i_1 = I_1 - I_2 = I_1 - I_2 = \frac{1}{9} \text{ A}$$



$$V_{oc} = 1.5i_1 \times 100 + 200(21 + 1.5i_1)$$

$$= 1.5 \cdot \frac{1}{9} \times 100 + 200\left(-0.5 + 1.5 \times \frac{1}{9}\right)$$

$$V_{oc} = 38.889V = V_{th}$$

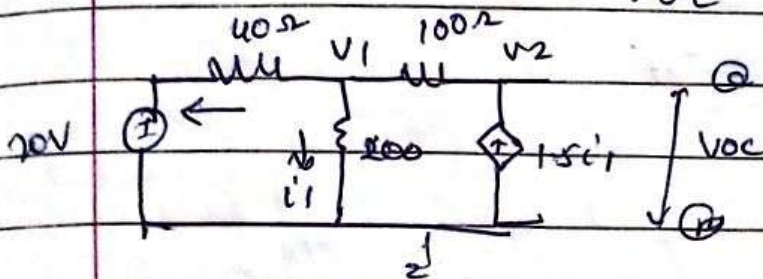


At node V_1 .

$$\frac{V_1 - 20}{40} + \frac{V_1}{200} + \frac{V_1 - V_2}{100} = 0$$

At node V_2 $\frac{V_2 - V_1}{100} - 1.5i_1 = 0$
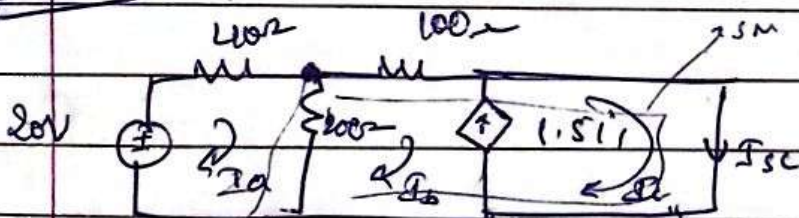
$$\frac{V_1}{200} = i_1 \quad \& \quad V_2 = V_{oc} = ?$$



$$I_c = I_{sc}$$

$$-I_a + i_1 + I_b = 0$$

$$I_b - I_a = -i_1 \quad \text{--- (A)}$$

$$-I_b - 1.5i_1 + I_c = 0$$

$$I_c - I_b = 1.5i_1 \quad \text{--- (B)}$$

$$20 - 40I_a - 200I_a + 200I_b = 0$$

$$-240I_a + 200I_b = -20 \quad \text{--- (C)}$$

$$I_a = \frac{3}{16} A$$

$$-200I_b + 200I_a - 100I_b = 0$$


$$-300I_b + 200I_a = 0$$

$$I_b = 1/8 A$$

$$i_1 = \frac{1}{16} \quad ; \quad I_{sc} = 1.5i_1 + I_b = \frac{7}{32} = 0.218A$$

verify
using
nodal
analysis

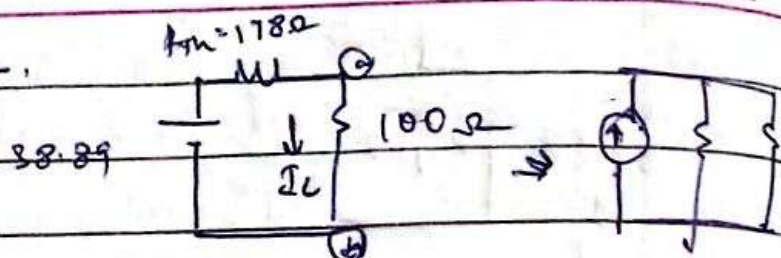
$$R_{Th} = \frac{V_{OC}}{I_{SC}} = 178 \Omega$$



$$P_L = R_L I_L^2 = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L = 1.96 \text{ W}$$

$$= \underline{\underline{13.89 \text{ W}}}$$

④ Maximum Power Transmission Theorem

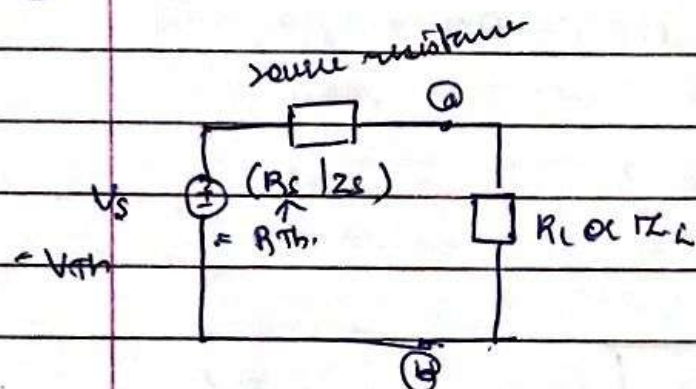

① When source & load are purely resistive (R_S & R_L)

② When source & load are an impedance (Z_S) & the load is purely resistive (R_L)

③ When the source & load are impedance (Z_S & Z_L)

$$Z_S = (R_S + j X_S)$$

$$Z_S = R_S + j X_S$$

$$Z_{load} = R_{load} + j X_{load}$$


④ Maximum power is transferred to load when $R_L = R_S = R_{Th}$.

⑤ Maximum power will be transferred to load

when $R_L = R_s + jX_s = \sqrt{R_s^2 + X_s^2}$

- c) Max power will be transferred to Z_L when
 $Z_L = Z_s^* = (R_s - jX_s)$

when source & load are purely resistive.

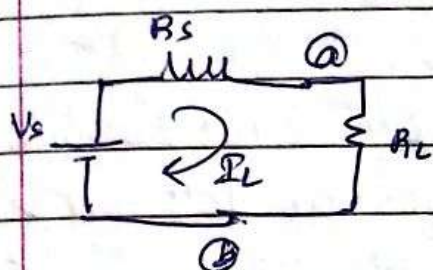

$$P_L = I_L^2 \cdot R_L = \left(\frac{V_s}{R_s + R_L} \right)^2 R_L \quad (1)$$

$$= \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2}$$

To determine the condition for M.P. transfered to load
 Let us diff with respect to R_L & equate to zero

$$\frac{dP_L}{dR_L} = 0; \quad \frac{(R_s + R_L)^2 \cdot V_s^2 \cdot 1 - V_s^2 \cdot R_L \cdot 2(R_s + R_L)(1)}{(R_s + R_L)^4} = 0$$

$$V_s^2 [R_s^2 + R_L^2 + 2R_s R_L - 2R_L R_s - 2R_L^2] = 0$$

$$V^2 [R_s^2 - R_L^2] = 0.$$

$$\text{As } V^2 \neq 0 \quad ; \quad \text{Hence } R_s^2 - R_L^2 = 0$$

$$R_s = R_L \quad (2)$$

Condition for maximum power transfer


Substitute in (1)

$$P_{L_{\max}} = \frac{V_s^2 \cdot R_s}{(2R_s)^2} = \frac{V_s^2}{4R_s} = \frac{V_s^2}{4R_L} \quad (3)$$

usually given circuit will be reduced to Thevenin's ckt, $V_t = V_{Th}$, $R_t = R_{Th}$. Then, condition for max power transfer in the load can be written as $R_L = R_{Th}$.

$$P_{L_{max}} = \frac{V_{Th}^2}{4 R_{Th}}$$

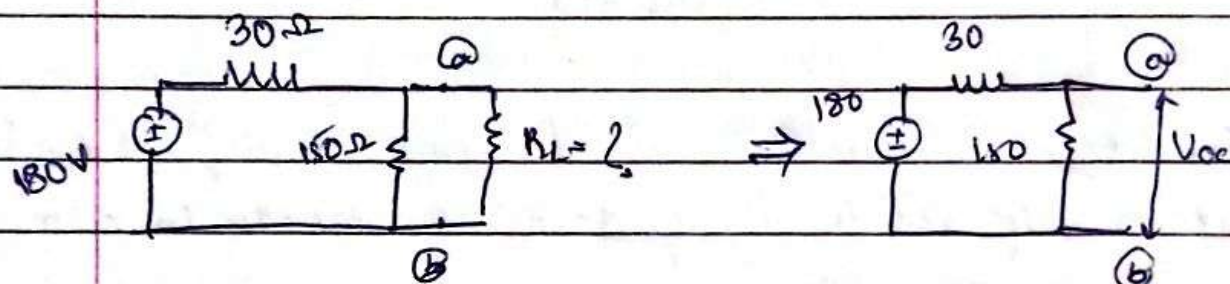- Find the value of R_L that will result in max power transfer in the load for the foll network & also determine the value of max power to load



$$180 - 30i - 150i = 0$$


$$180 = 180i$$

$$i = 1A$$

$$V_{Th} = 150V$$

$$R_{Th} = 25\Omega$$


$$\frac{30 \parallel 150}{= 25\Omega}$$

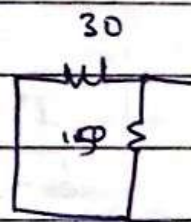

$$R_{Th} = R_L = 25\Omega$$

$$P_L = \frac{(150)^2}{4 \times 25} = 3 \times 255W$$

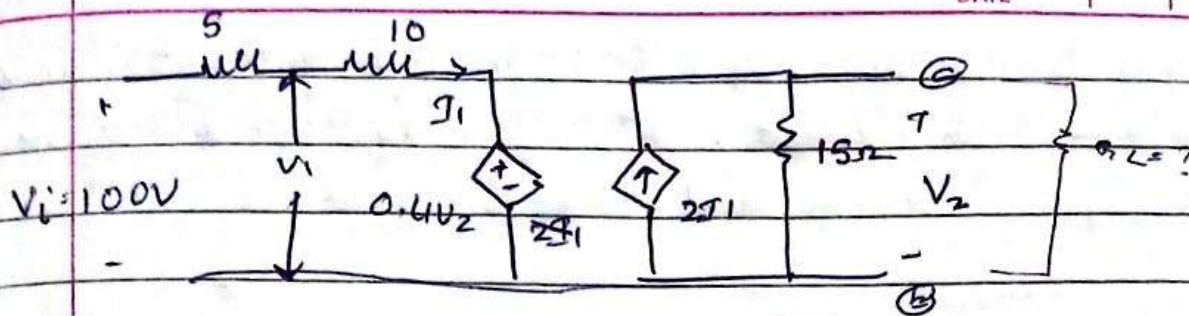- Find the value of R_L which is to be connected b/w A & B terminals to absorb max power in the foll ckt.



$$V_2 = V_{oc} = 2I_1 \times 15 = 30I_1.$$


$$100 - I_1 \times 15 - 0.4V_2 = 0.$$

$$100 - 15I_1 - 0.4 \times 30I_1 = 0$$

$$27I_1 = 100$$

$$I_1 = \frac{100}{27} = 3.704 A$$
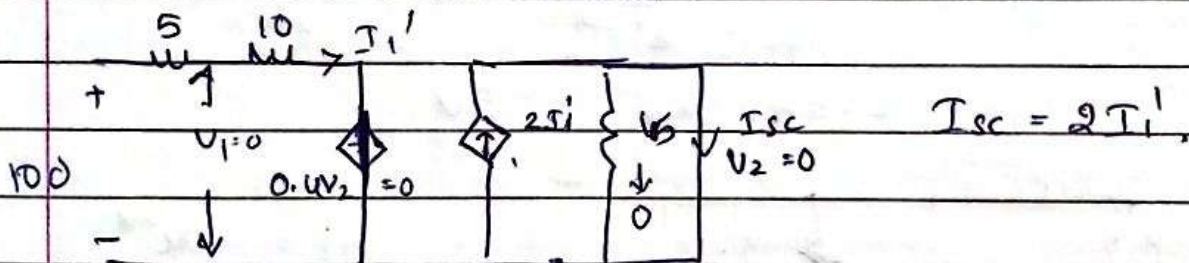
$$V_{oc} = V_2 = V_{th} = 30I_1 = 111.12 V.$$



$$I_1' = \frac{100}{15} = 6.67 A$$


$$I_{sc} = 2 \times 6.67 = 13.34 A$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{th}}{I_{sc}} = \frac{111.12}{13.34} = 8.33 \Omega = R_L \text{ for}$$

$$\text{max power transfer. } P_{Lmax} = \frac{(V_{th})^2}{4R_{th}} = \frac{111.12^2}{4 \times 8.33}$$

$$= 370.02 W$$

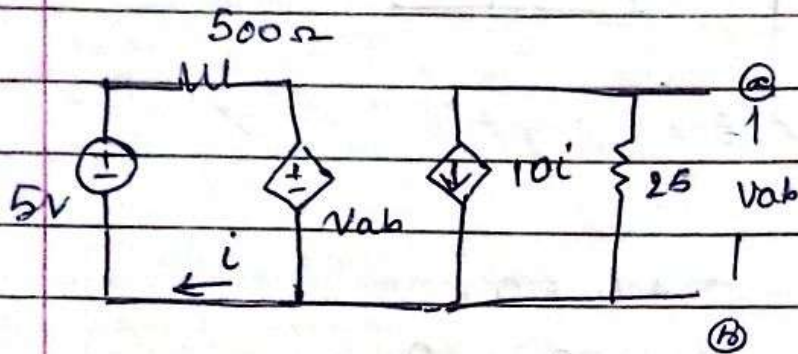- 6 Find Norton's eq lkt on left of the terminals a & b. Also deriv. theorem's eq lkt & det max ~~the~~ power transferred across load connected at a & b.




$$V_{ab} = V_{th} = -25 \times 10i = -250i.$$

$$5 - 500i - V_{ab} = 0.$$

$$5 - 500i + 250i = 0$$


$$i = \frac{5}{250} = 0.02 \text{ A}$$
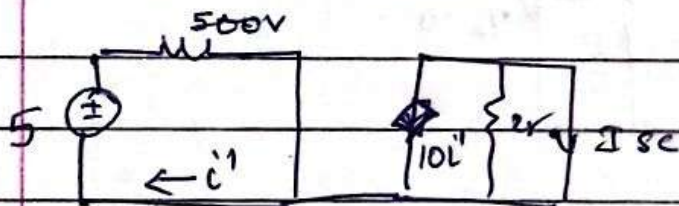
$$V_{ab} = -250 \times 0.02 = -5 \text{ V}$$




$$I_{sc} = 10i'$$
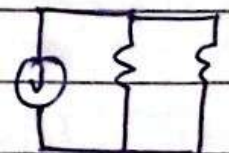
$$I_{sc} = 10 \times \frac{5}{500} = 0.1 \text{ A}$$



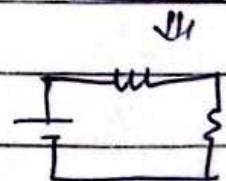
$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{-5}{0.1} = -50 \Omega$$



$$P_{max} = \frac{(5)^2}{4 \times 50} = \frac{25}{200} = 0.125 \text{ W}$$

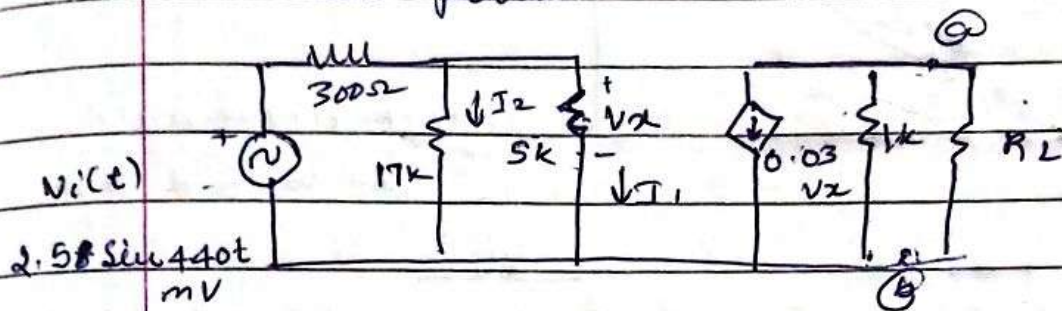- Full ckt is BJT model in CE mode. Determine the load resistance value through which BJT amplifier can supply max power & also determine the value of the max power.



$$V_{th} = 0.03 V_{z} \text{ K.}$$

$$2.58 - 300i - 17i = 0.$$

$$V_1 - \frac{2.58}{300} + \frac{V_1}{17} + \frac{V_1 - V_{z}}{5} = 0.$$

$$2.58 - 300i - \frac{17}{386}i = 0.$$

$$296.14i = 2.58$$

$$i = 8.71 \mu\text{A.}$$


$$V = 8.5 \times 3.86$$

$$V = 3.86 \times 10^3 \times 0.6 \times 10^{-6}$$

$$I_1 = \frac{I \times 17k}{17k + 5k} = 0.464 \mu\text{A}$$

$$V_{z} = I_1 \times 6k = 2.32 = 2.32 \sin(440t) \text{ mV}$$

$$V_m = V_{z} \times 0.03 = 0.696$$

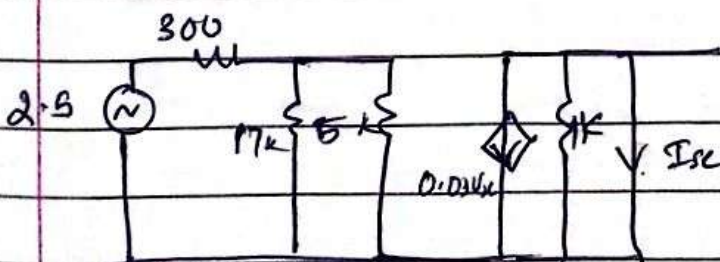

$$I_{sc} = -0.03 V_{z}$$


$$I_1 = \frac{2.5}{4.16 \times 10^3} = 0.6 \times 10^{-3}$$

$$I_{sc} = 0.0$$


$$R_{th} = \frac{0.696}{0.696} = 1k.$$

$$P_{max} = 1.211 \sin^2(440t) \mu\text{W.}$$

5]

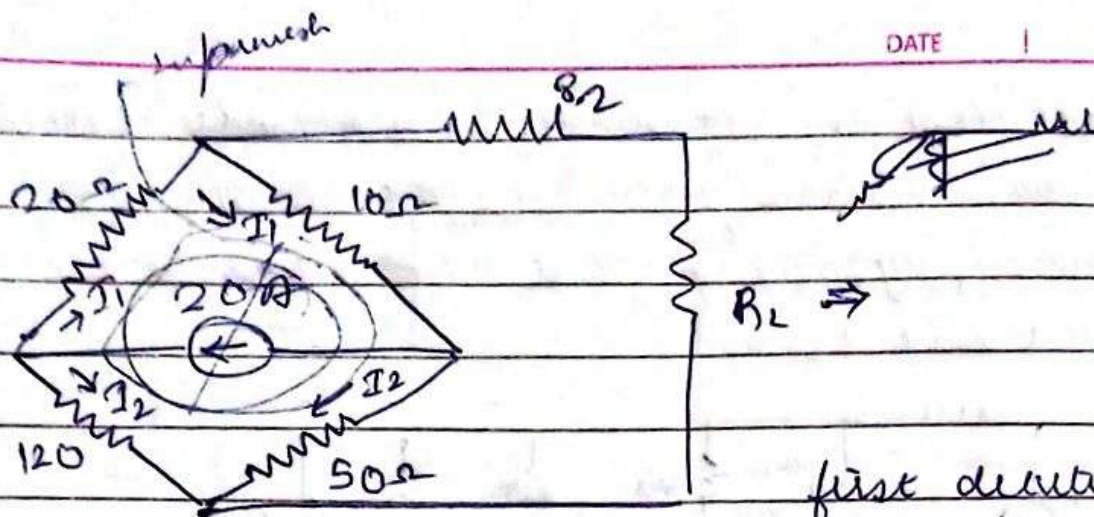

first debranch
2A to find R_{Th}

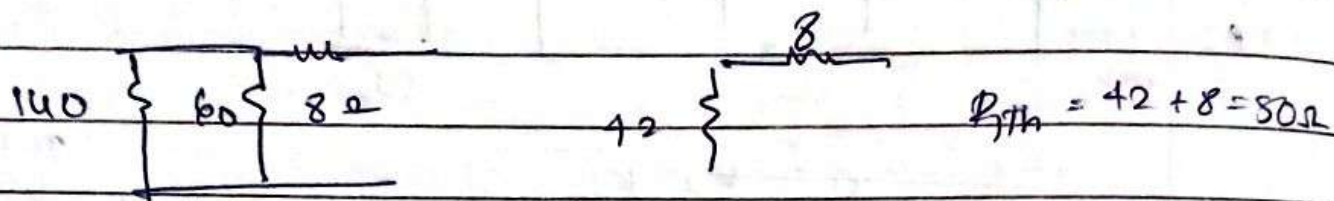

Supermesh,

$$I_1 - I_2 - 20 = 0$$

$$I_1 - I_2 = 20 \rightarrow \text{Constraint equation}$$

$$I_1 = 17A \quad I_2 = -3A$$


$$20I_1 + 10I_1 + 50I_2 + 120I_2 = 0$$

$$30I_1 + 170I_2 = 0$$

$$I_1 = +17 \quad I_2 = -3A$$


$$V_{ab} = 10 \times 17 - 3 \times 50$$

$$= \underline{\underline{20V}}$$

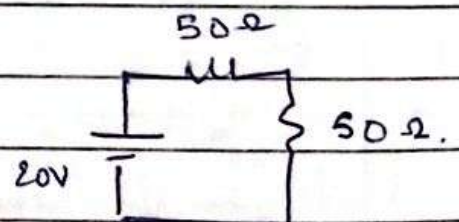

$$P_{max} = \frac{400}{4 \times 50} = \underline{\underline{2W}}$$

Reciprocity Theorem or Principle.

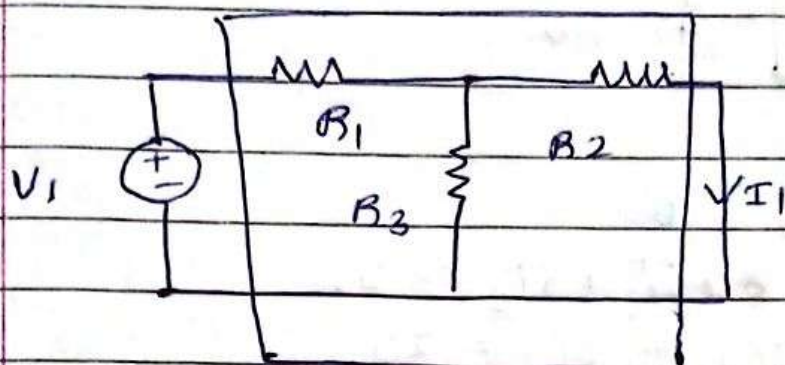

linear, bilateral


& vice versa.

$$\frac{V_1}{I_1} = \frac{V_1'}{I_1'}$$

$V \rightarrow$ Excitation


or $I_1 = I_1'$

$I \rightarrow$ Response

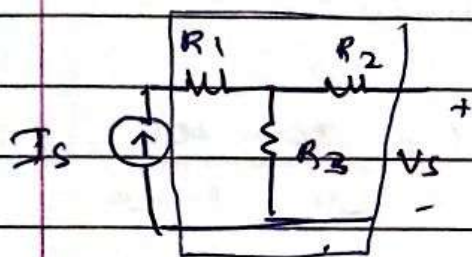


$I \rightarrow$ excitation

$V \rightarrow$ Response

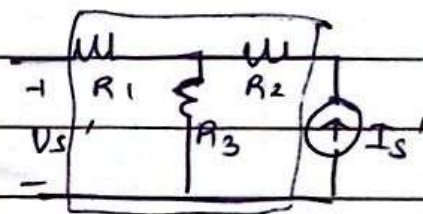

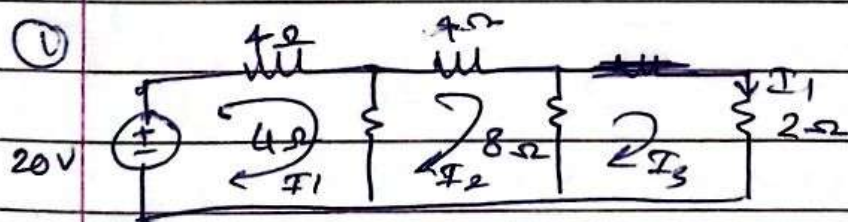- Find the current in 2Ω resistor & verify reciprocity theorem



$$20 - 4i_1 - 4(i_1 - i_2) = 0.$$


$$20 - 4i_1 - 4i_1 + 4i_2 = 0 \Rightarrow 20 = 8i_1 - 4i_2$$

$$-4i_2 + 4i_1 - 4i_2 - 8i_2 + 8i_3 = 0.$$

$$-16i_2 + 4i_1 + 8i_3 = 0.$$

$$-8i_3 + 8i_2 - 2i_3 = 0 \Rightarrow -10i_3 + 8i_2 = 0.$$
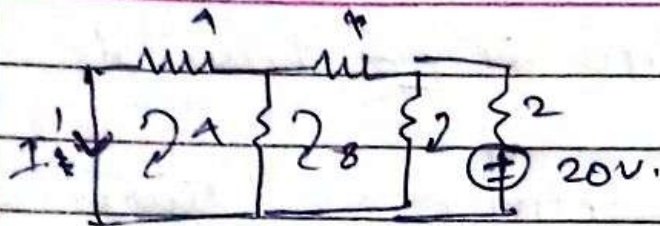
$$i_1 = 3.19 \quad i_2 = 1.31 \quad i_3 = 1.052A.$$



$$-8i_1' + 4i_2' = 0.$$

$$-16i_2' + 8i_1' + 8i_3' = 0.$$

$$-8i_3' - 2i_2' + 8i_2' = 20.$$

$$i_1' = 1.052 \text{ A}$$

Reciprocity principle is verified.

$$\frac{20}{I \times 1.052} = 20 = \frac{20}{I' \times 1.052}; \quad \frac{20}{I' \times 1.052} = 20 = \frac{20}{I \times 1.052} = I' = 0.92$$