

Linear Integrated Circuits


19EECC203

Unit: III

Chapter No: 06


Non-Linear Applications - Data Converters

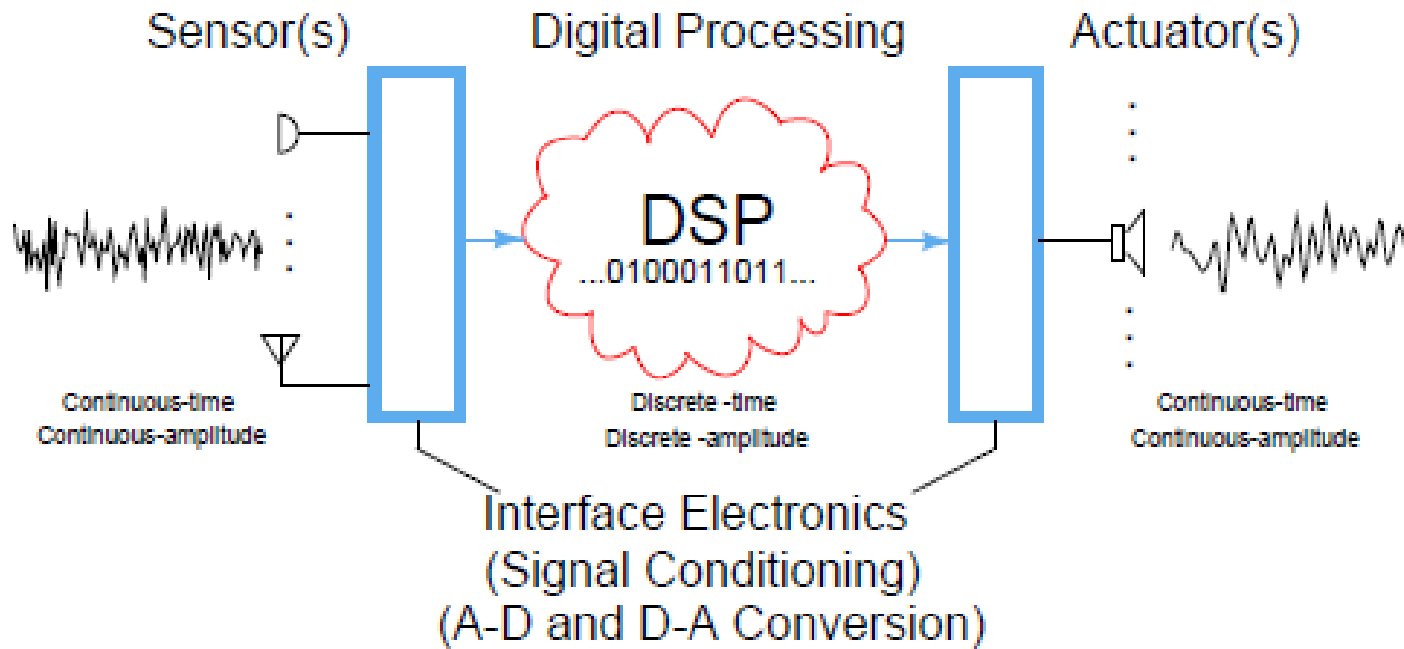Resource Person: Dr Sujatha Sanjay Kotabagi



Data converter circuits (ADC and DAC) are essential blocks for interfacing the analog world and digital systems.

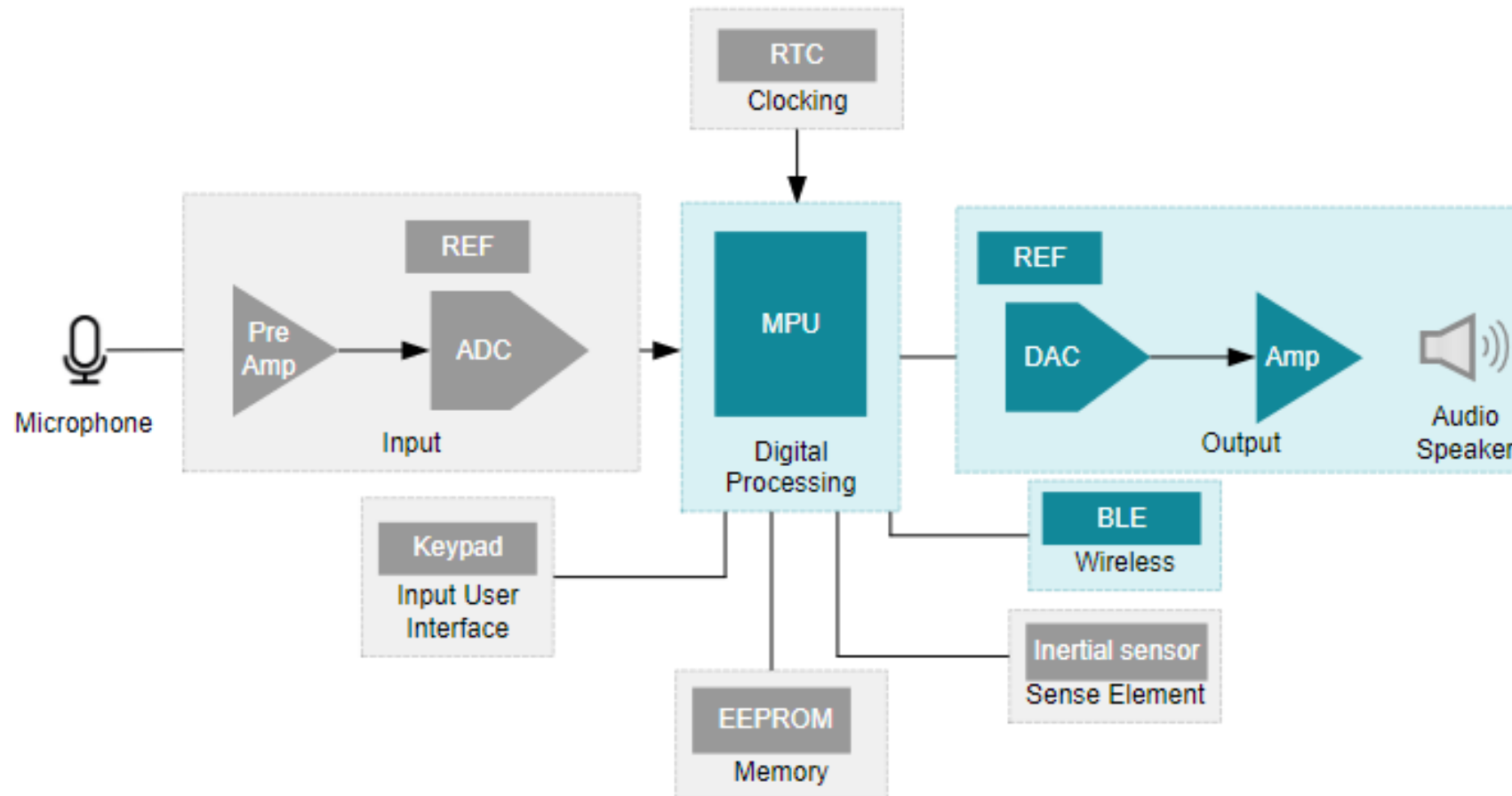Data Converters for Audio Range Applications



- *Applications such as wireless communications and digital audio and video have created the need for cost-effective data converters that will achieve higher speed and resolution.*
- *The needs required by digital signal processors continually challenge analog designers to improve and develop new ADC and DAC architectures.*
- *There are many different types of architectures, each with unique characteristics and different limitations.*

Types of Data converters


DACs

1. *Resistor String*
2. *R-2R*
3. *Current Steering*
4. *Cyclic*
5. *Pipeline*

ADCs

1. *Flash*
2. *Pipeline*
3. *Integrating - single slope
- dual slope*
4. *SAR*

Resistor String DAC

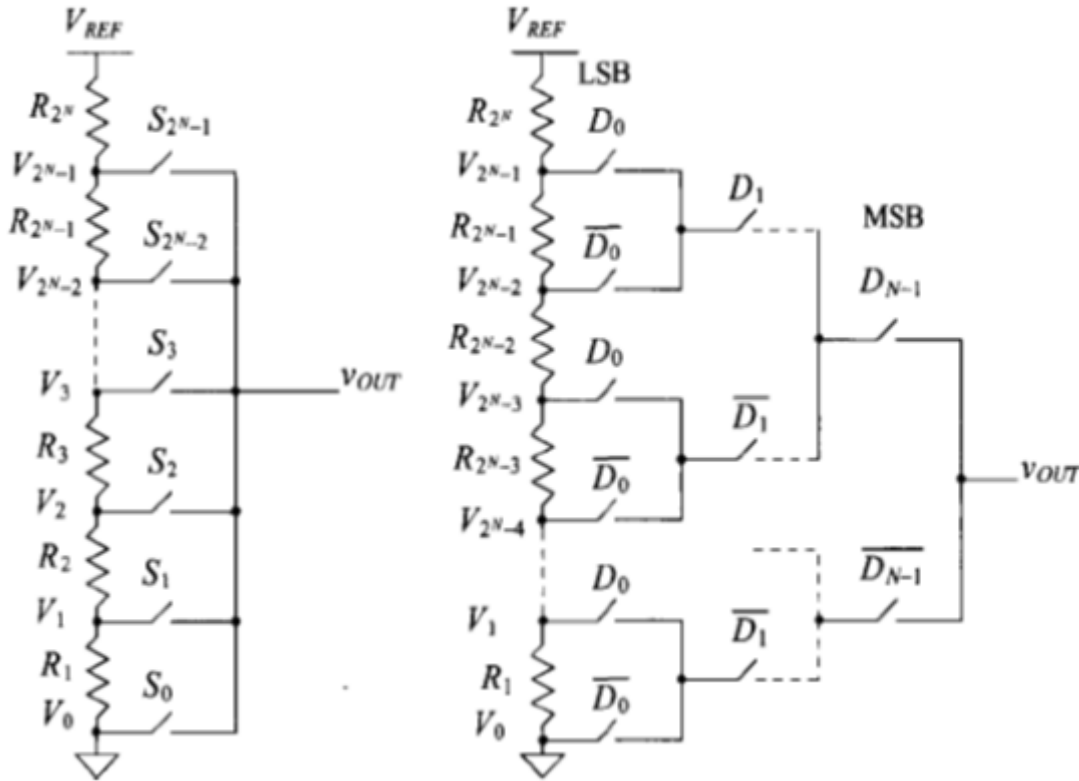


1. Resistor string of 2^N identical resistors and switches.
2. $N:2^N$ decoder is required to provide the 2^N signals to control the switches.
3. The analog output is simply the voltage division of the resistors at the selected tap.
4. $2^N - 1$ switches are off and one switch is on.
For larger resolutions, a large parasitic capacitance appears at the output node, resulting in slower conversion speeds.
5. Alternative for the resistor-string DAC is a binary switch array which ensures that the output is connected to at most N switches that are on and N switches that are off, thus increasing conversion speed.

Ex. Design a 3 bit converter with $V_{REF} = 5\text{ V}$ and maximum power dissipation of the converter of 5 mW

$$I_{MAX} = \frac{5 \times 10^{-3} \text{ W}}{5 \text{ V}} = 1 \text{ mA}$$


$$R = \frac{1}{8} \cdot \frac{5 \text{ V}}{1 \text{ mA}} = 625 \Omega$$

$$D_2 D_1 D_0 = 100 \text{ or } 4_{10}$$

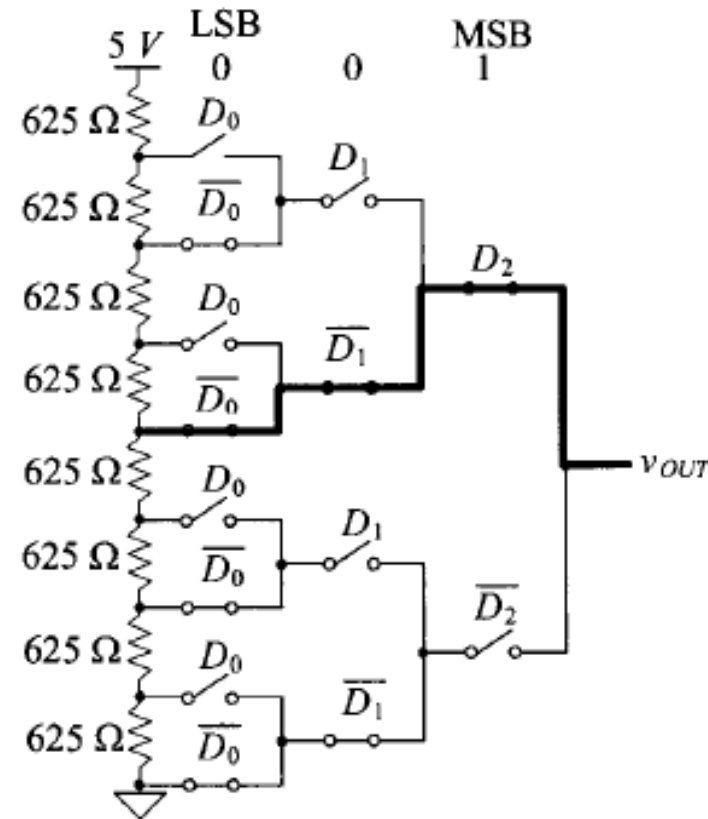

$D_2 D_1 D_0$	v_{OUT}
000	0
001	0.625
010	1.25
011	1.875
100	2.5
101	3.125
110	3.75
111	4.375

R-2R Ladder Network

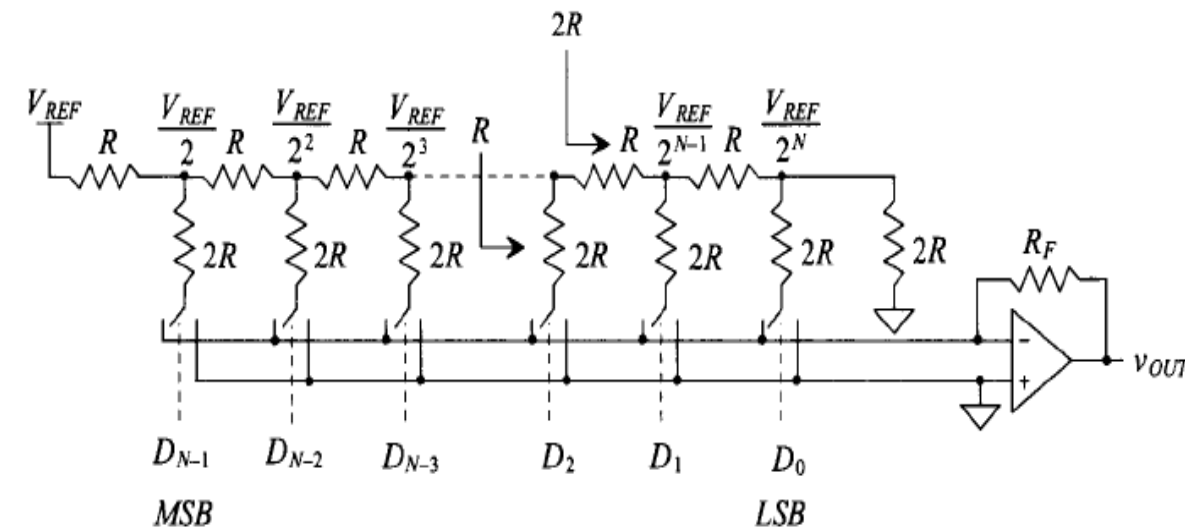


$$v_{OUT} = -i_{TOT} \cdot R_F$$

$$i_{TOT} = \sum_{k=0}^{N-1} D_k \cdot \frac{V_{REF}}{2^{N-k}} \cdot \frac{1}{2R}$$

where D_k is the k -th bit of the input word with a value that is either a 1 or a 0.

 1. It is a network of resistors alternating in value of R and $2R$.
2. The resistance looking to the right of any node to ground is $2R$.
3. The digital input determines whether each resistor is switched to ground (non-inverting input) or to the inverting input of the op-amp.
4. Each node voltage is related to V_{REF} , by a binary-weighted relationship caused by the voltage division of the ladder network.
5. The total current flowing from V_{REF} is constant, since the potential at the bottom of each switched resistor is always zero volts (either ground or virtual ground).

Ex. Design a 3-bit DAC using an R-2R architecture with $R = 1\text{ k}\Omega$, $R_F = 2\text{ k}\Omega$, and $V_{REF} = 5\text{ V}$. Assume that the resistances of the switches are negligible. Determine the value of i_{TOT} for each digital input and the corresponding output voltage, v_{OUT} .




$D_2 D_1 D_0$	i_{TOT} (mA)	v_{OUT} (V)
000	0	0
001	0.3125	-0.625
010	0.625	-1.25
011	$0.625 + 0.3125 = 0.9375$	-1.875
100	1.25	-2.5
101	$1.25 + 0.3125 = 1.5625$	-3.125
110	$1.25 + 0.625 = 1.875$	-3.75
111	$1.25 + 0.625 + 0.3125 = 2.1875$	-4.375

$$D_2 D_1 D_0 = 001 \quad i_{TOT} = \frac{V_{REF}}{8} \cdot \frac{1}{2000} = 0.3126\text{ mA}$$

$$v_{OUT} = -(0.3126\text{ mA})(2000\text{ }\Omega) = -0.625\text{ V}$$

Current Steering DAC

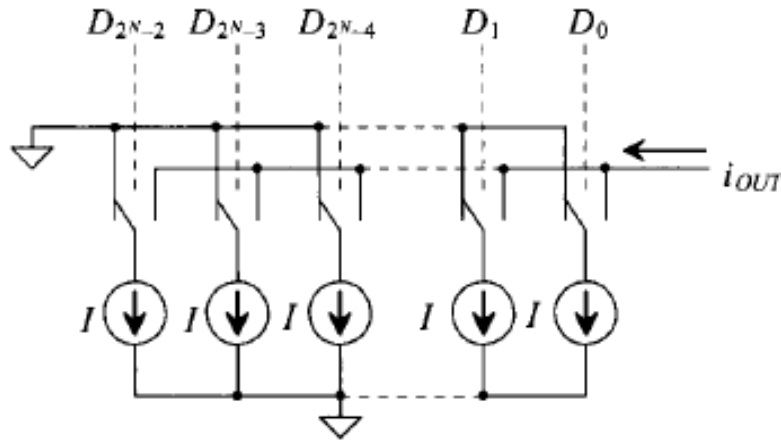Another DAC method uses current throughout the conversion. Known as current steering, this type of DAC requires precision current sources that are summed in various fashions.



A generic current-steering DAC.


1. This configuration requires a set of current sources, each having a unit value of current, I .
2. Since there are no current sources generating i_{OUT} when all the digital inputs are zero, the MSB, D_{2^N-1} , is offset by two index positions instead of one. For a 3-bit converter, seven current sources will be needed, labeled from D_0 to D_6 .
3. The binary signal controls whether or not the current sources are connected to either i_{OUT} or some other summing node (in this case ground).
4. The output current, i_{OUT} , has the range of

$$0 < i_{OUT} < (2^N - 1)I$$

and can be any integer multiple of I in between.

 
5. There are $2^N - 1$ current sources, the digital input will be in the form of a thermometer code.

A current-steering DAC using binary-weighted current sources.



- 1. This architecture uses binary-weighted current sources, thus requiring only N current sources of various sizes*
- 2. The input code can be a simple binary number with no thermometer encoder needed.*


Cyclic DAC

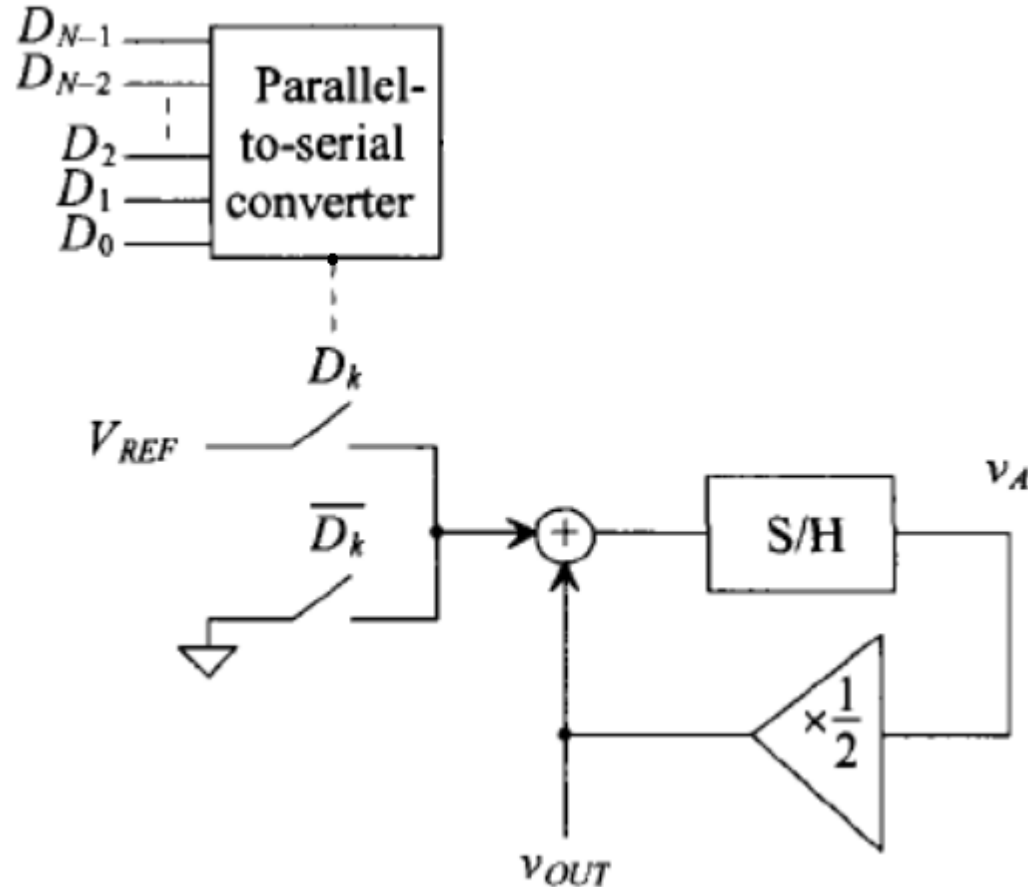

- 1. Inputs are read in serial fashion (PISO)*
- 2. Summer adds V_{REF} or ground to the feedback signal depending on the input bits.*
- 3. An amplifier with a gain of 0.5 feeds the output voltage back to the summer*
- 4. The output at the end of each cycle depends on the value of the output during the cycle before.*
- 5. The conversion is performed one bit at a time, resulting in N cycles for each conversion.*

$$v_{OUT}(n) = \left(D_{n-1} \cdot V_{REF} + \frac{1}{2} \cdot v_A(n-1) \right) \cdot \frac{1}{2} \quad \text{and} \quad [v_A(0) = 0 \text{ V}].$$

Pipeline DAC

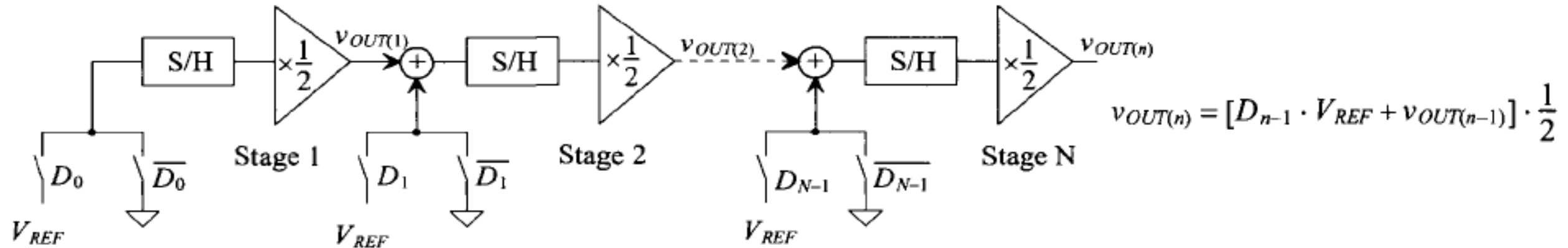

1. Extend the cyclic converter to N stages, where each stage performs one bit of the conversion-----Pipeline DAC


2. As each stage works on one conversion, the previous stage can begin processing another.

\therefore Initial N clock cycle delay and there after one conversion per cycle

Operation of each stage:



- If the input bit is a 1, add V_{REF} to the output of the previous stage, divide by two, and pass the value to the next stage.*
- If the input bit is a 0, simply divide the output of the previous stage by two and pass along the resulting value.*

Flash ADC

 

 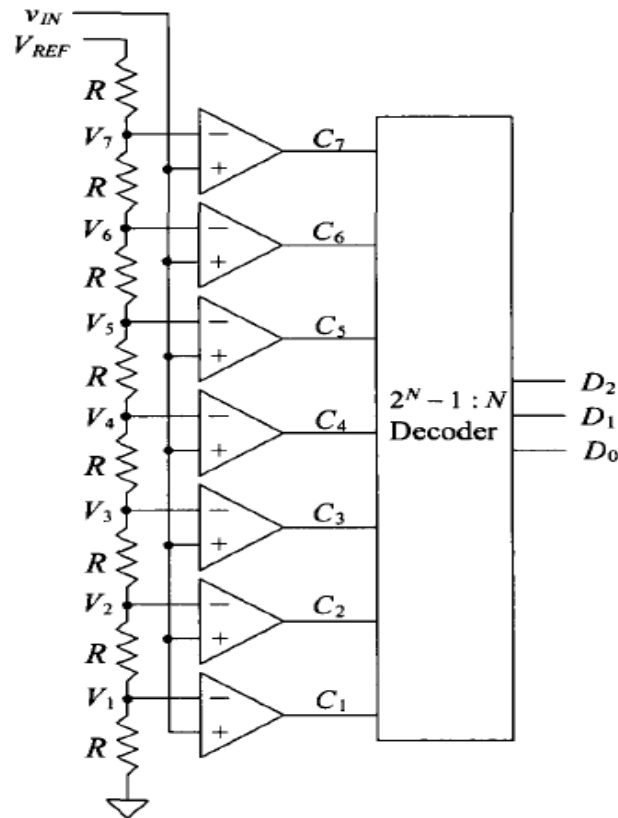1. One comparator per quantization level ($2^N - 1$) and 2^N resistors
2. The reference voltage is divided into 2^N values
3. The input voltage is compared with each reference value and results in a thermometer code at the output of the comparators
4. If $v_{in} < \text{value on the resistor string}$; comp output = all zeros
 $v_{in} > \text{value on the resistor string}$; comp output = all ones
5. $2^N - 1 : N$ digital thermometer decoder circuit converts the compared data into an N -bit digital word

Ex. Design a 3-bit Flash converter, listing the values of the voltages at each resistor tap, and draw the transfer curve for $v_{in}=0$ to 5 V. Assume $v_{REF}=5$ V. Construct a table listing the values of the thermometer code and the output of the decoder for $v_{in}=1.5$, 3.0, and 4.5 V.




v_{IN}	$C_7C_6C_5C_4C_3C_2C_1$	$D_2D_1D_0$
$0 \leq v_{IN} < 0.625$ V	0000000	000
$0.625 \text{ V} \leq v_{IN} < 1.25$ V	0000001	001
$1.25 \text{ V} \leq v_{IN} < 1.875$ V	0000011	010
$1.875 \text{ V} \leq v_{IN} < 2.5$ V	0000111	011
$2.5 \text{ V} \leq v_{IN} < 3.125$ V	0001111	100
$3.125 \text{ V} \leq v_{IN} < 3.75$ V	0011111	101
$3.75 \text{ V} \leq v_{IN} < 4.375$ V	0111111	110
$4.375 \leq v_{IN}$	1111111	111

$$V_1 = 0.625 \text{ V}, V_2 = 1.25 \text{ V}, V_3 = 1.875 \text{ V}, V_4 = 2.5 \text{ V}, V_5 = 3.125 \text{ V}, V_6 = 3.75 \text{ V}, V_7 = 4.375 \text{ V}.$$

Pipeline ADC



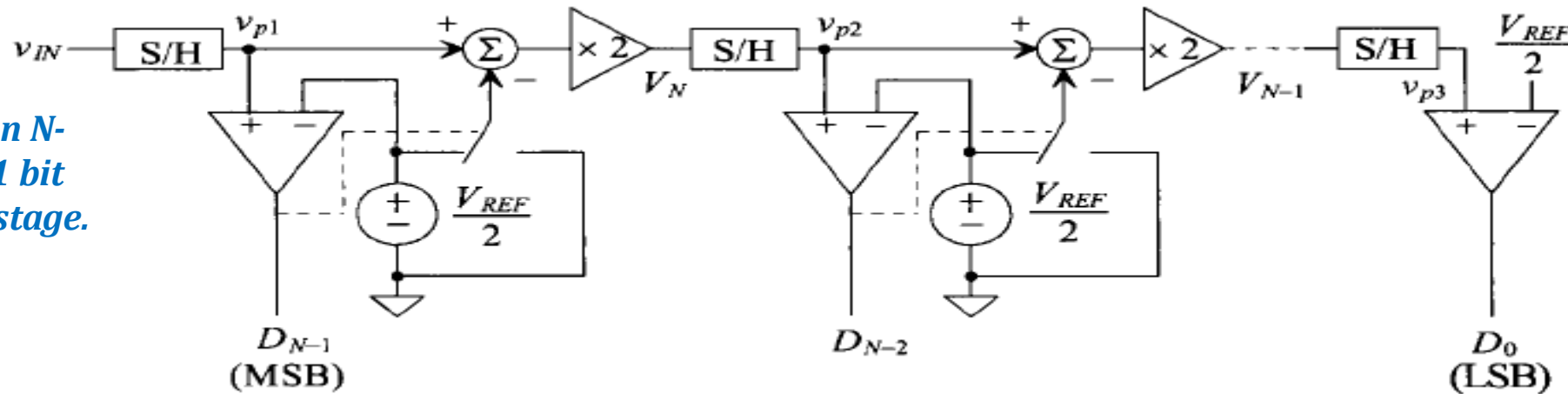
The pipeline ADC is an N -step converter, with 1 bit being converted per stage.



  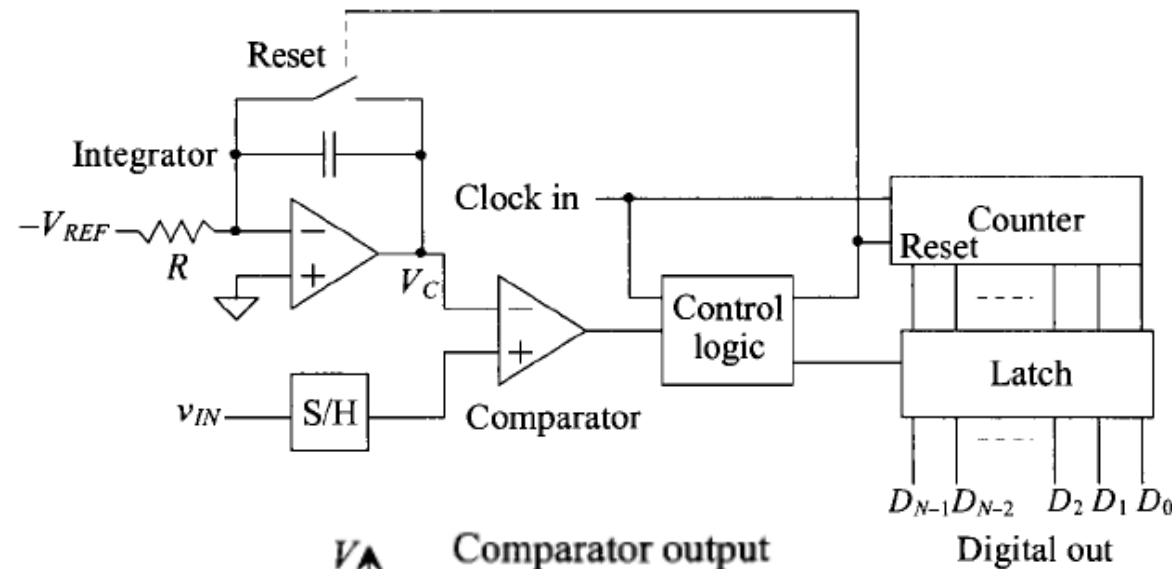1. After the input signal has been sampled, compare it to $\frac{V_{REF}}{2}$. The output of each comparator is the bit conversion for that stage.
2. If $v_{in} > \frac{V_{REF}}{2}$; comp output = 1; the difference $\left(v_{in} - \frac{V_{REF}}{2}\right)$ is amplified
If $v_{in} < \frac{V_{REF}}{2}$; comp output = 0; only v_{in} is amplified.
The output of each stage in the converter is referred to as the residue
3. Amplified signal is then passed to sample and hold of next stage

Integrating ADC



- *Conversion is performed by integrating the input signal and correlating the integration time with a digital counter.*
- *Two types of Integrating ADCs: Single slope- and Dual-slope ADCs*
- *Used in high-resolution applications, slow-speed, cost-conscious applications.*



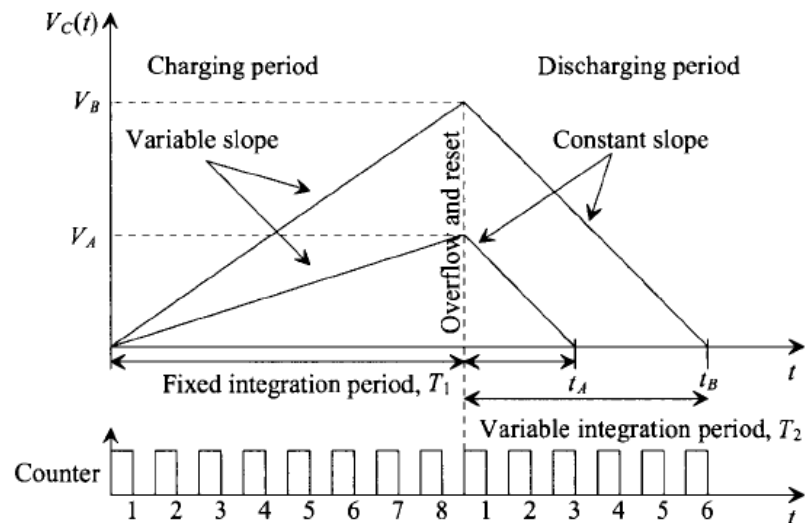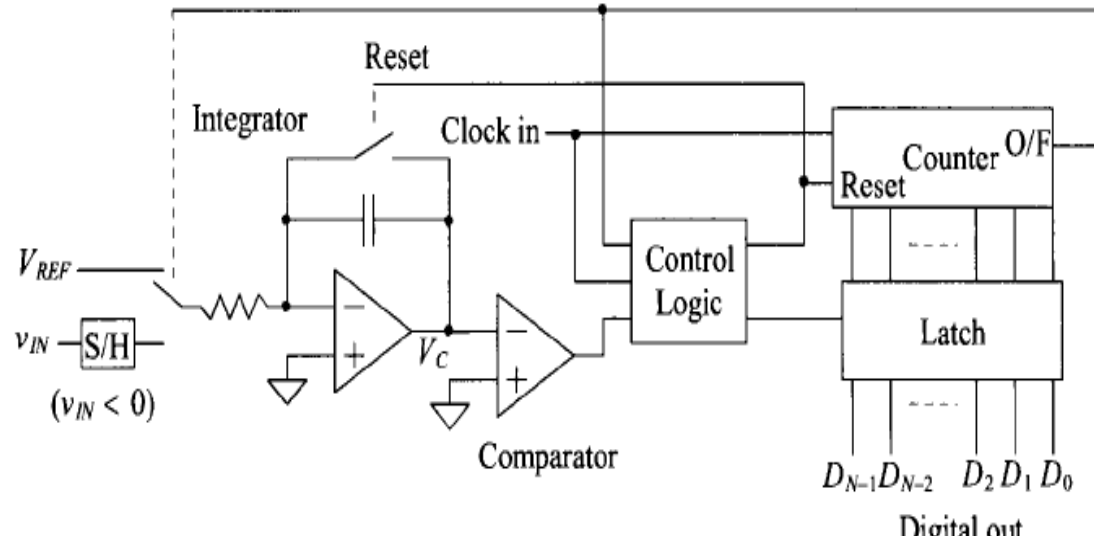1. The reference is a negative DC voltage, the output of the integrator should start at zero and linearly increase with a slope that depends on the gain of the integrator.
2. At the time when the output of the integrator surpasses the value of the S/H output, the comparator switches states, thus triggering the control logic to latch the value of the counter.
3. The control logic also resets the system for the next sample.
4. If the input voltage is at its full-scale value, the counter must increment to its maximum value of 2^N clock cycles. Thus, the clock frequency must be many times faster than the bandwidth of the input signal.


$$t_c = \frac{V_{IN}}{V_{REF}} \cdot 2^N \cdot T_{CLK}$$

$$f_{sample} = \frac{V_{REF}}{V_{IN} \cdot 2^N} \cdot f_{CLK}$$




1. Two integrations are performed, one on the input signal and one on V_{REF} .
2. The input voltage is assumed to be negative, and the output is a positive slope during the first integration (fixed length) dictated by counter.
3. After the counter overflows and is reset, the reference voltage is connected to the input of the integrator, whose output discharges to zero at a constant slope.
4. A counter again measures the amount of time for the integrator to discharge, thus generating the digital output.

Successive Approximation ADC

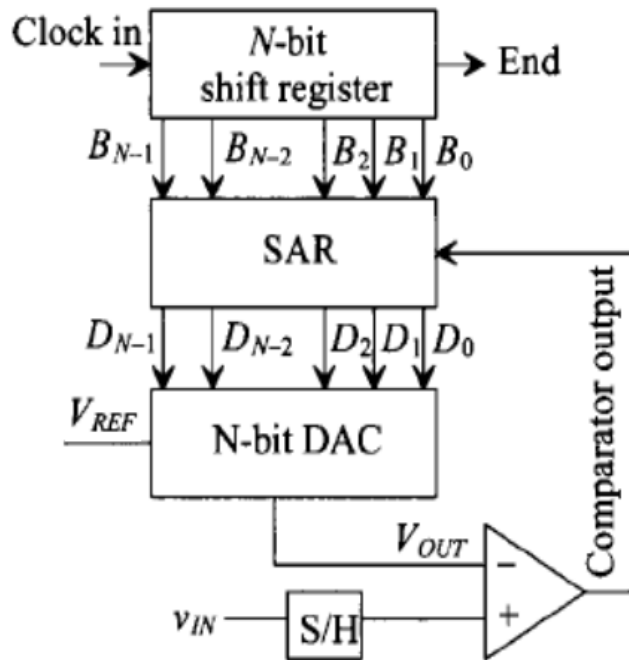

- *The successive approximation converter performs basically a binary search through all possible quantization levels before converging on the final digital answer.*
- *An N-bit register controls the timing of the conversion where N is the resolution of the ADC.*
- *v_{IN} is sampled and compared to the output of the DAC.*
- *The comparator output controls the direction of the binary search, and the output of the successive approximation register (SAR) is the actual digital conversion.*


Algorithm

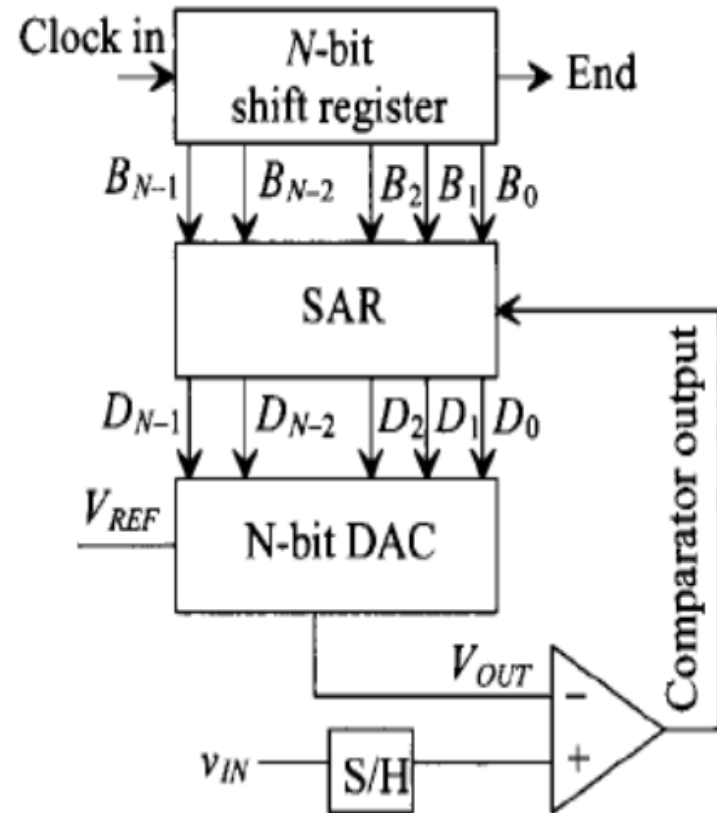

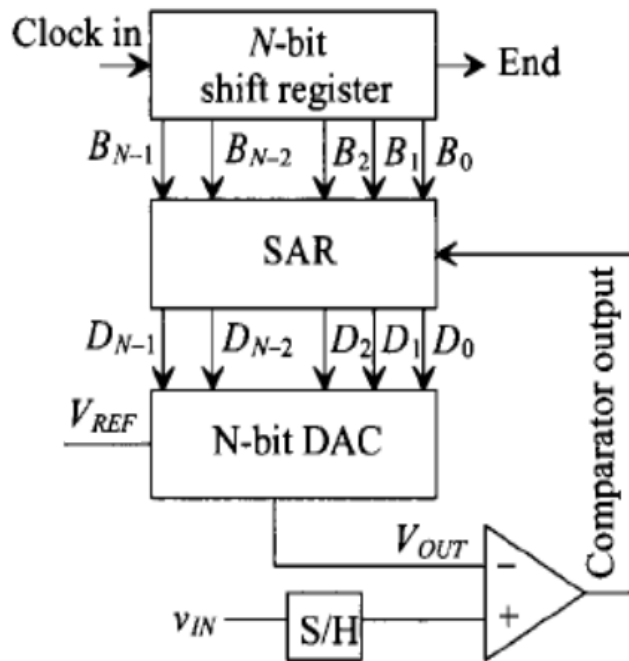1. A 1 is applied to the input of the shift register. For each bit converted, the 1 is shifted to the right 1-bit position. $B_{N-1} = 1$ and B_{N-2} through $B_0 = 0$.
2. The MSB of the SAR, D_{N-1} , is initially set to 1, while the remaining bits, D_{N-2} through D_0 , are set to 0.
3. Since the SAR output controls the DAC and the SAR output is 100...0, the DAC output will be set to $\frac{V_{REF}}{2}$.
4. If $\frac{V_{REF}}{2} > v_{IN}$; comparator output = 0 and the comparator resets D_{N-1} to 0.
If $\frac{V_{REF}}{2} < v_{IN}$; comparator output = 1 and the D_{N-1} remains a 1.
 D_{N-1} is the actual MSB of the final digital output code.
5. The 1 applied to the shift register is then shifted by one position so that B_{N-2} while the remaining bits are all 0.
6. D_{N-2} is set to a 1, D_{N-3} through D_0 remain 0, while D_{N-1} remains the value from the MSB conversion.

The output of the DAC = $\frac{V_{REF}}{4}$ (if $D_{N-1} = 0$) or $\frac{3V_{REF}}{4}$ if ($D_{N-1} = 1$)

Perform the operation of a 3-bit SAR ADC with $V_{REF}=8$. Show the binary search algorithm of the converter for $v_{IN} = 5.5V$ and $2.5V$.



Step	v_{IN}	$B_2B_1B_0$	$D_2D_1D_0$	V_{OUT}	Comp Out	$D_2D_1D_0$
T1	5.5	100	100	$1/2 V_{REF} = 4V$	0	100
T2	5.5	010	110	$(1/2 + 1/4)V_{REF} = 6V$	1	100
T3	5.5	001	101	$(1/2 + 1/8)V_{REF} = 5V$	0	101

Step	v_{IN}	$B_2B_1B_0$	$D'_2D'_1D'_0$	V_{OUT}	Comp Out	$D_2D_1D_0$
T1	2.5	100	100	$1/2 V_{REF} = 4V$	1	000
T2	2.5	010	010	$1/4 V_{REF} = 2V$	0	010
T3	2.5	001	011	$(1/4 + 1/8)V_{REF} = 3V$	1	010

Reference

CMOS Circuit Design, Layout, and Simulation

R. Jacob Baker

Thank you

Linear Integrated Circuits

19EECC203

Unit: III
Chapter No: 06
Non-Linear Applications

Faculty Incharge: Dr Sujata Sanjay Kotabagi

Course Outcome (CO): Design and analyze the non-linear applications of Op-Amp for the given specifications.

PO1.3.1 - Apply fundamentals of Electrical engineering principles and laws

PO1.4.1 - Apply principles of electronic device

PO1.4.2 - Ability to understand electronic circuits

PO2.1.2 - Identify engineering systems, variables, and parameters to solve the problems


PO2.1.4 - Identify the mathematical, engineering and other relevant knowledge that applies to a given problem

Non-Linear Mode Applications

- Output is saturated: $v_o = \pm V_{o,sat}$
- Differential input is : $v_d \geq \frac{\pm V_{o,sat}}{A}$
- Dominant positive feedback: $\beta_- < \beta_+$

 
Problems on Non-Linear Applications of Op-Amp

P01: Determine the oscillation frequency and the condition to sustain oscillations for the circuit shown. Assume the Op-Amp to be ideal.



$$\text{Gain, } |A| = \frac{R_1}{R_2} + 1$$
 
$$\text{Feedback network is, } \therefore \beta = \frac{V_f}{V_o}$$



$$\therefore V_f = V_o \frac{\left(R \parallel \frac{1}{2sC}\right)}{\left(R \parallel \frac{1}{2sC}\right) + \left(2R + \frac{1}{sC}\right)}$$

$$F = \frac{V_f}{V_o} = \frac{sCR}{4s^2C^2R^2 + 5sCR + 1}$$

For oscillations to occur

$$[A\beta] = 1$$

$$[A] = \frac{1}{\beta}$$

$$\therefore \text{So, } \left(1 + \frac{R_1}{R_2}\right) = \frac{4sC^2R^2 + 5sCR + 1}{sCR}$$

Put, $s = j\omega$, to get frequency of oscillations.

$$\therefore j\omega CR(R_1 + R_2) = R_2 + j\omega 5CRR_2 - 4\omega^2C^2R^2R_2$$



Let us compare imaginary parts

$$\therefore \omega CR(R_1 + R_2) = \omega 5CRR_2$$

$$\begin{aligned} \omega CRR_1 &= \omega 5CRR_2 \\ R_1 &= 4R_2 \text{ and} \\ 0 &= R_2 - 4\omega^2C^2R^2R_2 \\ \omega &= \frac{1}{2CR} \end{aligned}$$

  Problems on Non-Linear Applications of Op-Amp

P02: Calculate the load current through R_L





$$V_P = V_N \text{ [Virtual short]}$$

$$I_0 = I_C = \left(\frac{\beta}{\beta + 1} \right) I_E = \left(\frac{\beta}{\beta + 1} \right) \frac{V_{ref}}{R}$$

  Problems on Non-Linear Applications of Op-Amp

P03: Plot the transfer characteristics of the circuit shown. Assume ideal diodes



$$V_i = L_{tp} \text{ when } V_o = -10V$$

$$L_{tp} = \frac{-10 \times 2K}{(2+2)K}$$

$$= \frac{-20}{4}$$


$$L_{tp} = -5V$$

$$V_i = U_{tp} \text{ when } V_o = +10V$$

When diode D_2 is Forward bias



$$U_{tp} = \frac{10 \times 2K}{0.5k + 2K} = \frac{20}{2.5}$$

$$U_{tp} = 8V$$

 

  Problems on Non-Linear Applications of Op-Amp

P04: A triangular wave which goes from -12V to +12V is applied to the inverting input of the Op-Amp. Calculate the voltage that switches between the non-inverting input.



From KCL : $I_1 + I_2 + I_3 = 0$

$$\frac{V_t - 15}{10k} + \frac{V_t + 15}{10k} + \frac{V_t - V_o}{10k} = 0$$

$$3V_t = V_o$$

$$V_t = \frac{V_o}{3} \dots\dots\dots (1)$$

Threshold depends on output

So, when $V_o = +15$


$$V_t = 15/3 = 5V.$$

When $V_o = -15$

$$V_t = \frac{-15}{3} = -5V$$

 Problems on Non-Linear Applications of Op-Amp

P05: In the voltage regulator circuit shown op-amp is ideal. BJT has $V_{BE} = 0.7V$ and $\beta=100$ and the Zener voltage is $4.7V$. Calculate the value of R to have a regulated voltage of $9V$



$$V^+ = V^- = 4.7V = V_R$$

Op-amp draws no current


$$\text{Hence } I_{1k\Omega} = I_R$$

$$\frac{9 - 4.7}{1k} = \frac{4.7}{R}$$

$$R = 1093 \Omega$$

 Problems on Non-Linear Applications of Op-Amp

P06: $V_{in} = 20V \pm 20\%$, $V_{out} = 10V$, Calculate the maximum power dissipation in Q_1 if load current through R_L is 200mA



$$I_1 = \frac{4}{10k}$$

$$I_1 = 0.4 \text{ mA}$$

KCL at output node

$$I_E = I_1 + I_L$$

$$= 200 \text{ mA} + 0.4 \text{ mA}$$

$$I_E = 200.4 \text{ mA}$$

$$I_C \approx I_E = 200.4 \text{ mA}$$

It is given, $V_{in} = 20V \pm 20\%$

For maximum power dissipation

$$V_{in} = 20 + \frac{20 \times 20}{100}$$

$$V_{in} = 24V$$

$$V_{in} = V_C = 24V$$

$$V_E = V_0 = 10V$$

$$\therefore V_{CE} = V_C - V_E = 24 - 10 = 14 \text{ V}$$

\therefore Maximum power dissipation



$$P_{max} = V_{CE} I_C$$

$$= 14 \times 200.4 \text{ m}$$

$$= 2.8056 \text{ W}$$

  Problems on Non-Linear Applications of Op-Amp

P07: Calculate the value of C to have a sinusoidal frequency of 1kHz



$$\frac{V_o - V_f}{R + X_c} = \frac{V_f}{R} + \frac{V_f}{X_c}$$

$$V_o = (R + X_c) \frac{(R + X_c)V_f}{R.X_c} + V_f$$

$$\frac{V_o}{V_o} = \frac{R/j\omega C}{R^2 - \frac{1}{\omega^2 C^2} + \frac{2R}{j\omega C} + \frac{R}{j\omega C}}$$

$$\frac{V_f}{V_o} = \frac{R}{j\omega CR^2 - \frac{j}{\omega C} + 3R}$$

For oscillators, imaginary part = 0



$$\omega CR^2 - \frac{1}{\omega C} = 0$$

$$\Rightarrow C = \frac{1}{\omega R}$$

$$C = \frac{1}{2\pi \times 1 \times 10^3 \times 1 \times 10^3} \\ = \frac{1}{2\pi} \mu F$$

  Problems on Non-Linear Applications of Op-Amp

P08: Calculate the ratio of R_2 to R_1 to have a sinusoidal frequency of f_0 kHz at $B(f) = \frac{V_f(f)}{V_0(f)} = \frac{1}{6}$



$$\frac{\beta V_0 - 0}{R_1} + \frac{\beta V_0 - V_0}{R_2} = 0$$

$$\frac{\beta V_0}{R_1} + \frac{\beta V_0}{R_2} - \frac{V_0}{R_2} = 0$$

$$\beta V_0 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_0}{R_2}$$

$$\beta \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{1}{R_2}$$

$$\beta \left[\frac{R_2 + R_1}{R_1 R_2} \right] = \frac{1}{R_2}$$

$$\frac{R_1 \left(1 + \frac{R_2}{R_1} \right)}{R_1} = \frac{1}{\beta}$$


$$1 + \frac{R_2}{R_1} = \frac{1}{\beta}$$

$$\text{Given } \frac{1}{\beta} = 6 \Rightarrow 1 + \frac{R_2}{R_1} = 6$$

$$\frac{R_2}{R_1} = 5; \quad R_2 = 5R_1$$

 Problems on Non-Linear Applications of Op-Amp

P09: Identify the circuit and explain the function of $100\text{k}\Omega$ resistor in series with two diodes connected back to back




Ans:

- **The circuit shown is a Wein Bridge Oscillator.**
- **To provide amplitude stabilization by preventing the op-amp going into saturation.
This will cause sinusoidal oscillations of fixed amplitude.**
- **When oscillations grow, diodes conduct, D1—positive cycle
D2—negative cycle.**
- **$22.1\text{k}\Omega$ will come in parallel with $100\text{k}\Omega$, thereby reducing the effective resistance in the feedback.**
- **Under equilibrium the loop gain will be unity.**

 Problems on Non-Linear Applications of Op-Amp



P10: Find the value of R^1 for generating sinusoidal oscillations. Also find the frequency of oscillations.



$$\text{Ans: } R^1 = 2R \quad \text{and} \quad \omega = \frac{1}{CR}$$

  Problems on Non-Linear Applications of Op-Amp

P11: Plot the transfer characteristics of the Precision Rectifier circuit shown.



Case (1):

$$i_1 + i_2 + i_3 = i$$

$$\frac{20}{4R} + \frac{V_i}{R} + \frac{V_o}{R} = i$$

If V_o is positive diode not conduct so $i = 0$.

$$\text{Then } \frac{20}{4R} + \frac{V_i}{R} + \frac{V_o}{R} = 0$$

$$5 + V_i + V_o = 0$$

$$\therefore V_o = -5 - V_i$$


$$\text{At } V_i = -10V$$

$$V_o = -5 + 10 = 5V$$

$$\text{At } V_i = -5V$$

$$V_o = -5 + 5 = 0V$$

 When $V_i > -5V$, D_1 - OFF, D_2 - ON are conducting
so, $V_o = 0V$.



Thank you